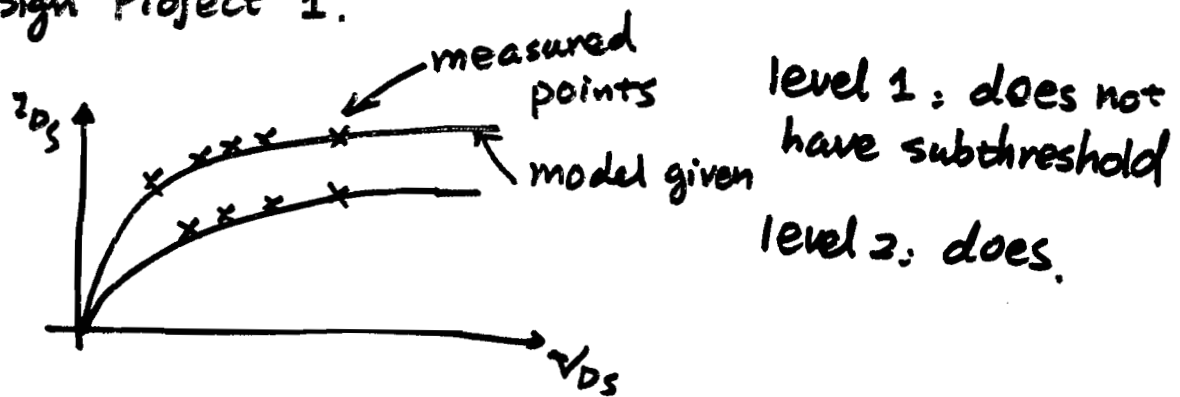


design Project 1.



Keep in mind, your measured points may be off from your model

This is the reason you have 10% off is fine!

The state of art is BSIM 5, 200 equations
you should also understand corners.


Common Source:

high Gain : $A_v = 100 \sim 1000$

(moderate gain : 5, 10

low gain : 1.2 ...)

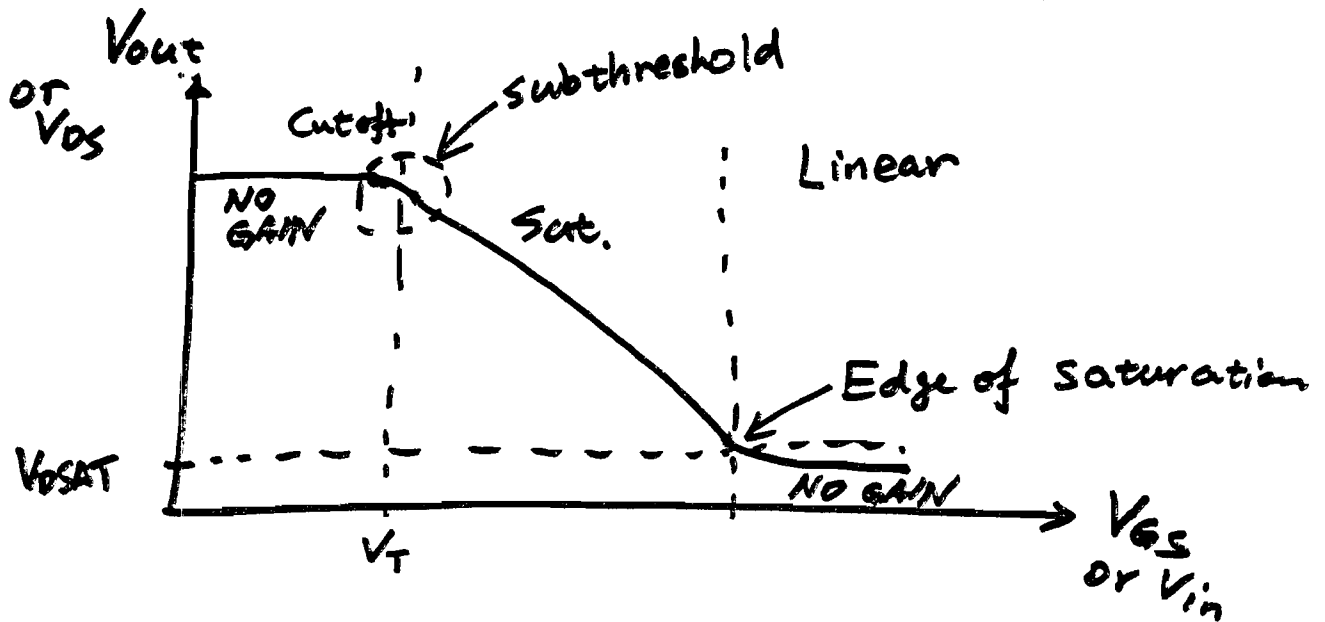R_{out} :
 { High : 10s of $M\Omega$
 moderate R_{out} : 10s of $K\Omega$, $K\Omega$
 low R_{out} : 10s Ω $< 100\Omega$





No Body effect $V_{SB} = 0$

$$V_{out} = V_{DD} - I_{DS} R_D$$

$I_{DS} = 0$ at cutoff, $I_{DS} \uparrow$ $V_{DS} \downarrow$
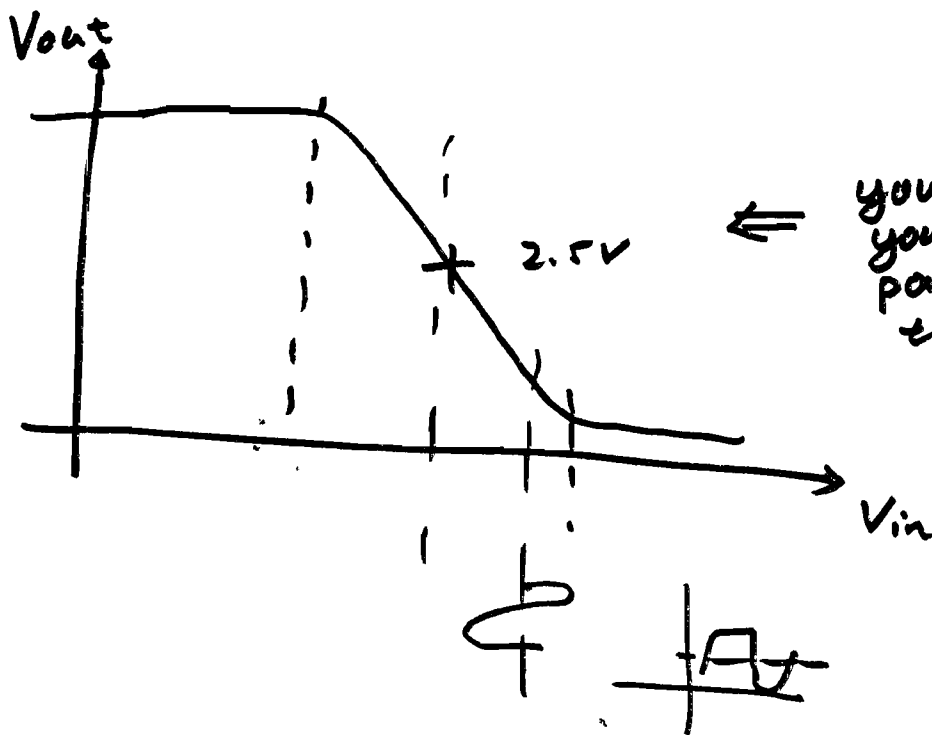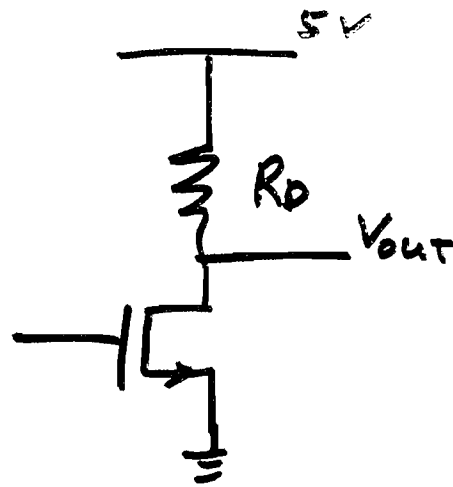
$$V_{DS} > V_{DSAT} = \left(\frac{2 I_{DS}}{k' \frac{W}{L}} \right)^{\frac{1}{2}}$$



you put your DC bias point in the middle to avoid clipping

$$R_D = 1k\Omega$$

V_{out} wish to be 2.5V.

$$\Rightarrow I_{DQ} = \frac{2.5V}{1k\Omega} = 2.5mA \quad \leftarrow \text{you want } I_{DQ} \text{ to be this}$$

$$\Rightarrow V_{GSAT} = \left(\frac{2I_{DQ}}{K' \frac{W}{L}} \right)^{\frac{1}{2}} = 3.08V$$

$$\hookrightarrow I_{DQ} = \frac{K' W}{2 L} \left(\underbrace{V_{in} - V_T}_{V_{GSAT}} \right)^2 (1 + \lambda V_{DS})$$

$\rightarrow 0.01$
 $\hookrightarrow 2.5V$
 $0.025 \ll 10\% \times 1V$

so you can forget $(I_D \rightarrow V_{DS})$

SP.4.

$$\Rightarrow I_{OS} = \frac{k' W}{2 L} \underbrace{(V_{IN} - V_T)^2}_{V_{DSAT}}$$

$$\Rightarrow V_{OSAT} = \left(\frac{2 I_{OS}}{k' \frac{W}{L}} \right)^{\frac{1}{2}} = 3.08$$


$$\Rightarrow \because V_{GS} - V_T = V_{OSAT}$$

$$\Rightarrow V_{GS} = V_{OSAT} + V_T = 4.08 \text{ V.}$$

$$\text{or } V_{IN} = 4.08 \text{ V.}$$


$$\Rightarrow \underline{V_{IN} = 4 \text{ V!}} \quad \text{it is possible}$$

Small signal analysis:

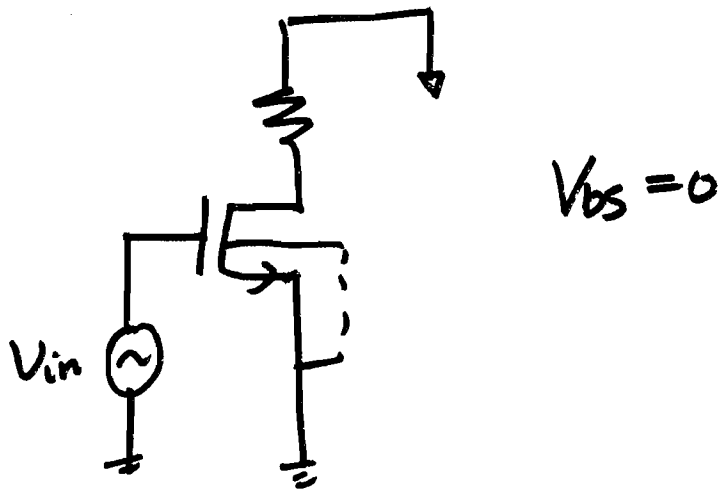

$$\text{So: } g_m = \sqrt{2k' \frac{W}{L} I_{DQ}}$$
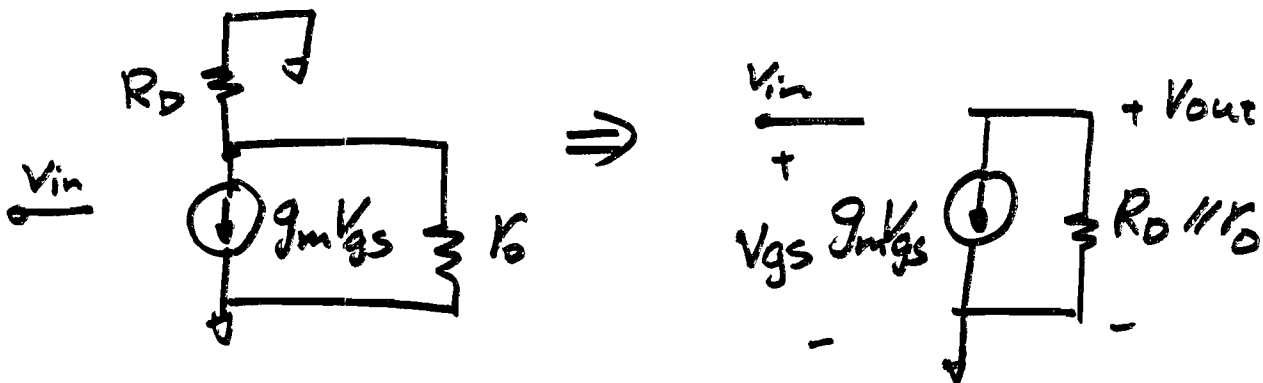
$$\Rightarrow r_o = \frac{1}{\lambda I_{DQ}} = \dots$$



$$V_{gs} = V_{in}$$

$$V_{out} = -g_m V_{gs} \cdot R_D \parallel r_o = -g_m (R_D \parallel r_o) V_{in}$$

$$A_v = \frac{V_{out}}{V_{in}}$$

LECT# 3.



SP-6

$r_o = 40k\Omega, R_D = 1k\Omega$

$R_D // r_o \approx R_D, g_m = 1.2 \times 10^{-3}$

$\Rightarrow A_V = 1.2$ too small Bad design


2-port and π -model
 G_m vs. g_m .

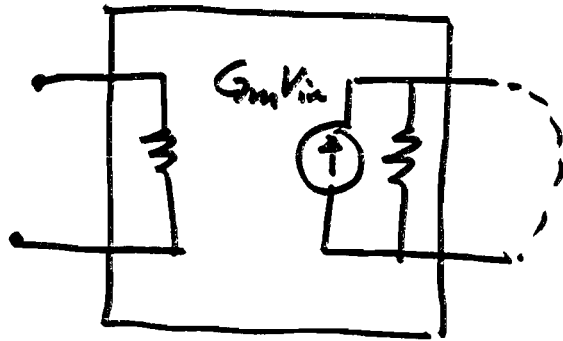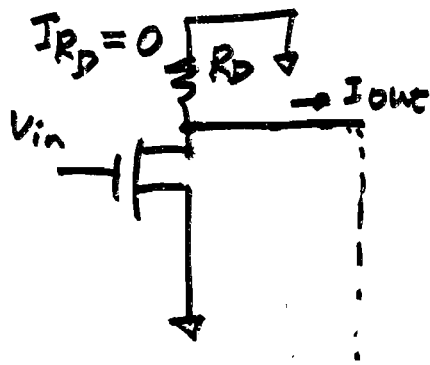

$I_{out} = g_m V_{in}$

short the output.


$G_m = \frac{i_{out}}{V_{in}} \Big|_{V_{out}=0} = -g_m$

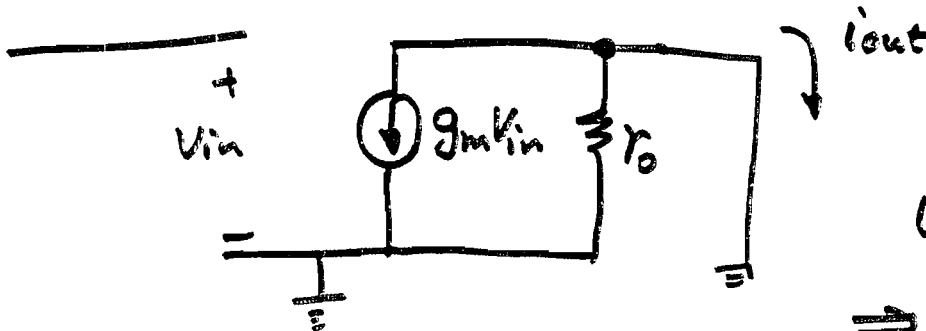

$i_{out} = -g_m V_{in}$


$\Rightarrow G_m = -g_m$

How to calculate R_{out} .

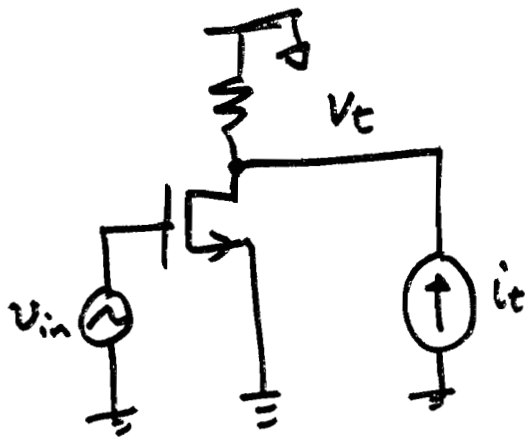

$$R_{out} = \frac{V_t}{i_t} \Big|_{\substack{IND-source=0 \\ V_{in}=0}}$$


Ohm meter

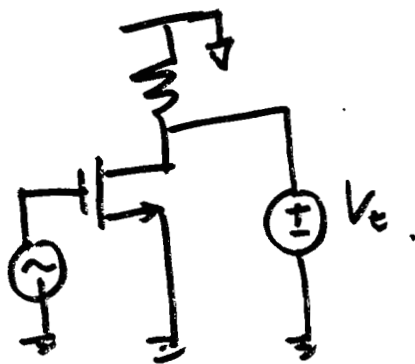

$$\Rightarrow R_{out} = \frac{V_t}{i_t} = R_D // R_L$$

You can do the same for R_{in}

$$\Rightarrow R_{in} = \infty$$

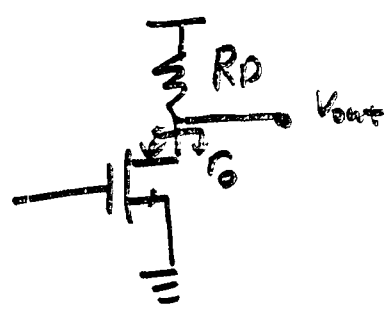

★

$$G_m = -g_m$$

$$R_{out} = R_D // r_o$$

$$R_{in} = \infty$$

$$A_v = G_m R_{out} = -g_m (R_D // r_o)$$

maximum gain you can have


for CS: $A_v = -g_m r_o \propto \frac{\sqrt{I_{os}}}{I_{os}} \sim \frac{1}{\sqrt{I_{os}}}$

$I_{os} \downarrow \Rightarrow A_v \uparrow$

It causes r_o more dependant on I_{os}
Not good!

bipolar is better! But cmos cheap.

DC analysis

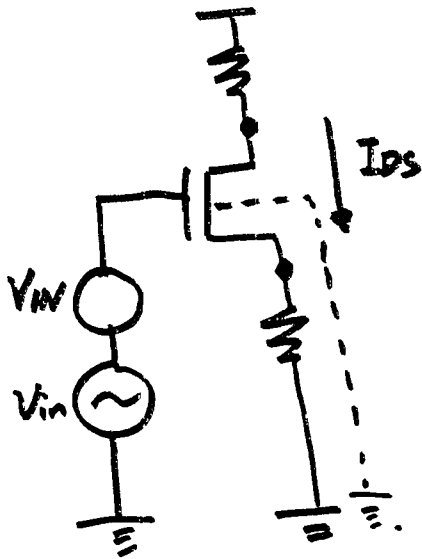

$$V_{DS} > V_{OSAT}$$

boundary EOS (Edge of Saturation)

$$\Rightarrow V_{OS} = V_{OSAT} \Rightarrow V_{OS} = V_{DD} - I_{DS}(R_D + R_S) = V_{OSAT}$$

$$\Rightarrow V_{DD} = V_{OSAT} + I_{DS}(R_D + R_S)$$


$$\Rightarrow \text{EOS. } V_{IN, EOS}$$

you want to set $V_{IN} = \frac{1}{2}(V_T + V_{IN, EOS})$



$$I_{DS} = \frac{1}{2} K' \frac{W}{L} (\underbrace{V_{GS}}_{V_{IN}} - V_T)^2 (\dots)$$

$\Rightarrow I_{DS}$ at DC.


Now small signal analysis

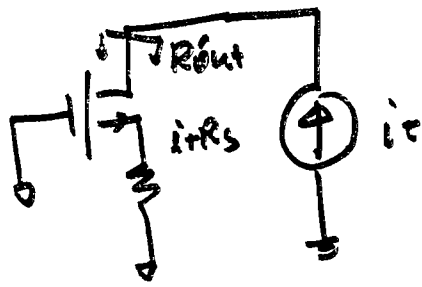
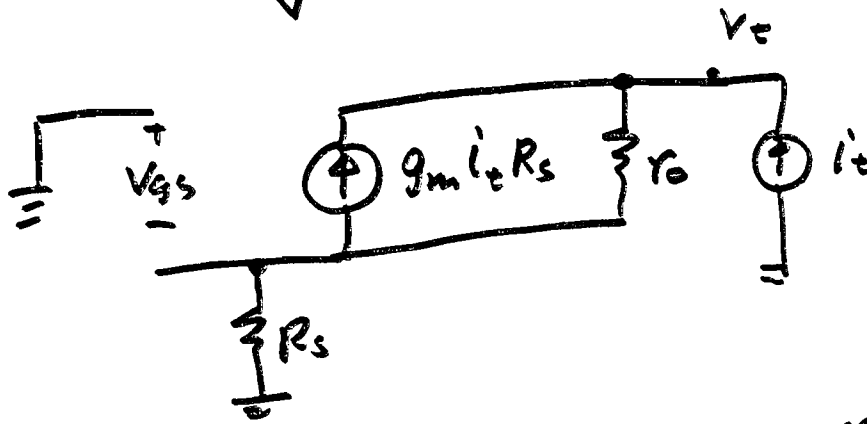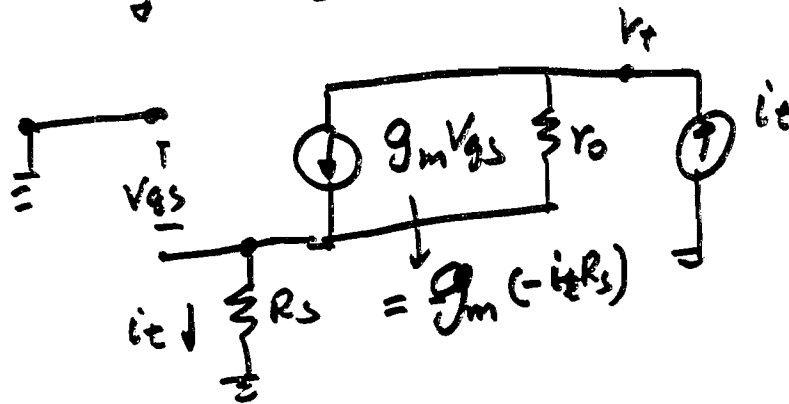
$$V_{gs} \neq 0 \Rightarrow V_g = 0, V_s \neq 0$$



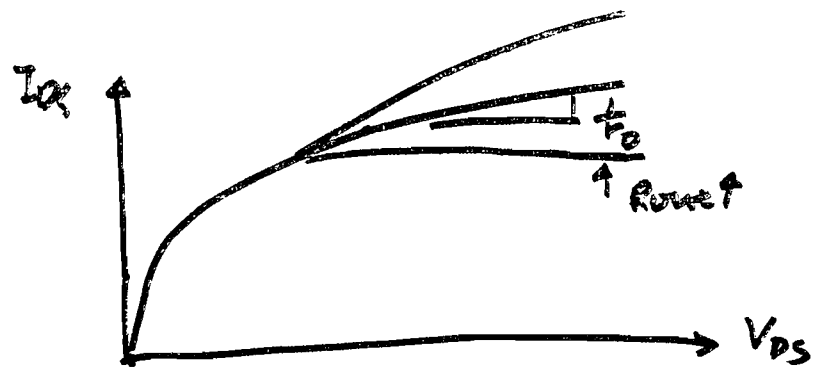- ① This voltage as source pumps current to drain!
- ② $V_t = V_{R_s} + V_{r_o} = i_t R_s + i_t g_m R_s r_o = i_t (R_s + g_m R_s r_o)$
 $\Rightarrow V_t = i_t (R_s + g_m R_s r_o)$
 Effectively, because of ①, you see a jump increase in R_{out} ! you improve R_{out} , why?




you can make it more like current source!

$$R_{out} = R_s + r_o [(1 + g_m (1 + \beta) R_s)] \parallel R_D !!!$$

$$A_v = G_m R_{out}$$

$$G_m = ?$$

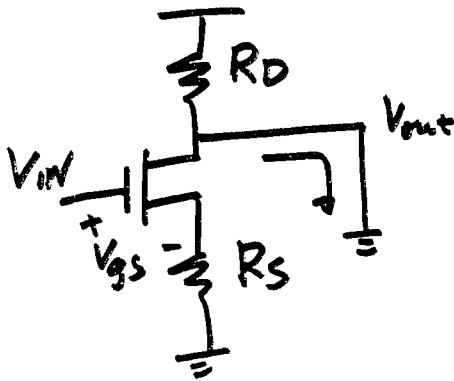

$$G_m = \frac{i_{out}}{v_m}$$

$$i_{ds} = g_m v_{gs} = -i_{out}$$

$$v_{R_s} = g_m R_s v_{gs}$$

$$v_{gs} = v_{in} - g_m R_s v_{gs}$$

$$v_{gs} (1 + g_m R_s) = v_{in}$$

$$\Rightarrow v_{gs} = \frac{v_{in}}{1 + g_m R_s}$$

$$\Rightarrow \boxed{G_m = \frac{-g_m}{1 + g_m R_s}}$$

$$r_o \gg R_s$$

$$R_{out} \doteq r_o \left[1 + \underbrace{g_m(1+\alpha)R_s}_{\gg 1} \right] \doteq g_m(1+\alpha)R_s r_o$$

$$A_v = G_m R_{out} = \frac{-g_m}{1+g_m R_s} (R_D \parallel g_m(1+\alpha)R_s r_o)$$

$$\text{if } R_D \ll g_m R_s r_o$$


(if R_D too big, you have ^{big} voltage chop)

$$A_v \doteq \frac{-g_m R_D}{1+g_m R_s} \doteq -\frac{R_D}{R_s}$$

$$A_v \doteq -\frac{R_D}{R_s}$$

very popular case

★

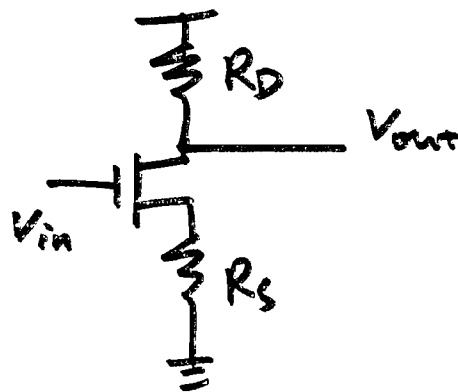


if well designed

$$A_v \doteq -\frac{R_D}{R_s}$$

① $g_m(1+\alpha)R_s \gg 1$

NO g_m

② $R_D \ll g_m R_s r_o$

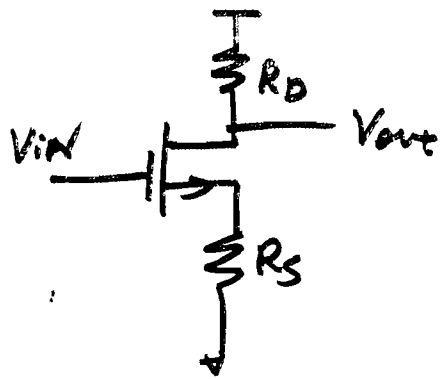

Under


$$g_m(1+\alpha)R_S \gg 1$$

if $R_D \ll g_m R_S r_o$


$$A_v \approx \frac{R_D}{R_S}$$

if $R_D \gg g_m R_S r_o$

$$A_v \approx -g_m r_o$$

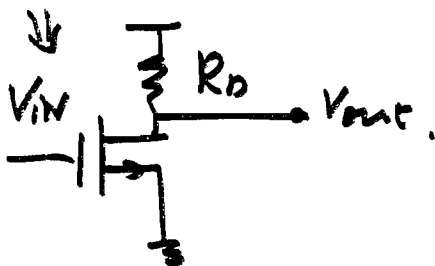


★ one important item

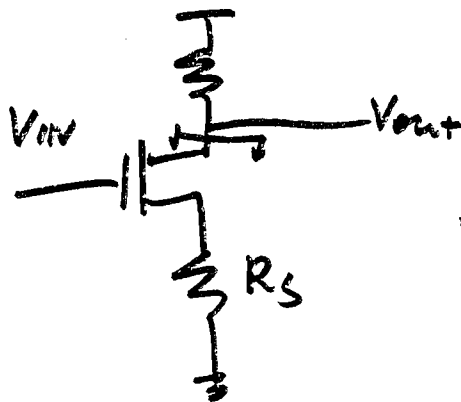

if you have R_S ,
 $R_{out} \uparrow$ by $g_m(1+\alpha)R_S$

$$R_{out} \approx g_m(1+\alpha)R_S r_o$$

Large signal

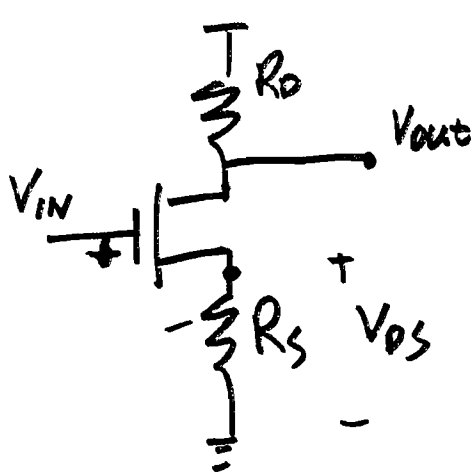

$$I_{DS} = \frac{V_{DD} - V_{out}}{R_D} \quad \checkmark$$

$$V_S = V_{R_S} = I_{DS} R_S$$

$$I_{DS} \Rightarrow V_{DSAT}$$

$$V_{IN} - V_T = V_{DSAT} \Rightarrow V_{IN} = V_T + V_{DSAT}$$

$$V_{DS} = V_{out} - V_{R_S}$$

$$V_{DSAT} \mid I_{DS} = \frac{V_{DD} - V_{out}}{R_D} = \frac{V_{DD} - (V_{DS} + V_{R_S})}{R_D}$$

~~$$V_{out} = A_v \cdot V_{in} = \frac{R_D}{R_S} \cdot (V_{DSAT} + V_T)$$

$$= \frac{R_D}{R_S} \cdot \frac{V_{DD} - V_{out}}{R_D}$$

$$= \frac{V_{DD} - (V_{DS} + V_{R_S})}{R_S}$$~~

$$V_{out} = \frac{V_{DD}}{2} \Rightarrow I_{DS} \Rightarrow V_{DSAT} \Rightarrow V_{IN}$$



you put R_S there, it's easy (easier)

to put transistor to sat region!

$$(I_{DS} \downarrow \Rightarrow V_{DSAT} \downarrow \Rightarrow V_{IN} = V_T + V_{DSAT})$$

①


Common gate

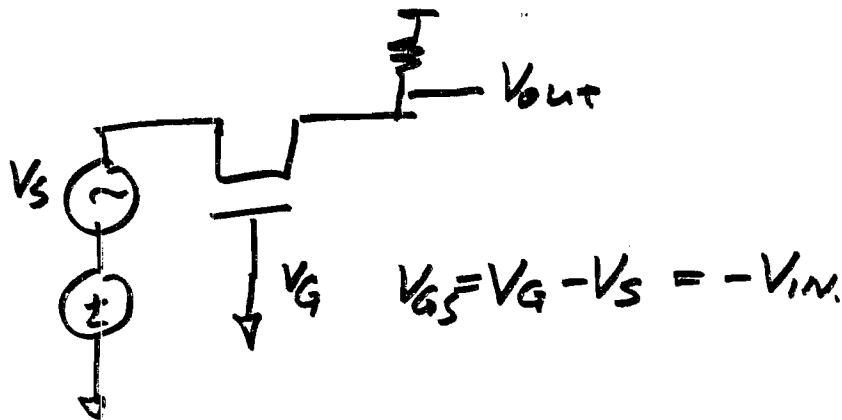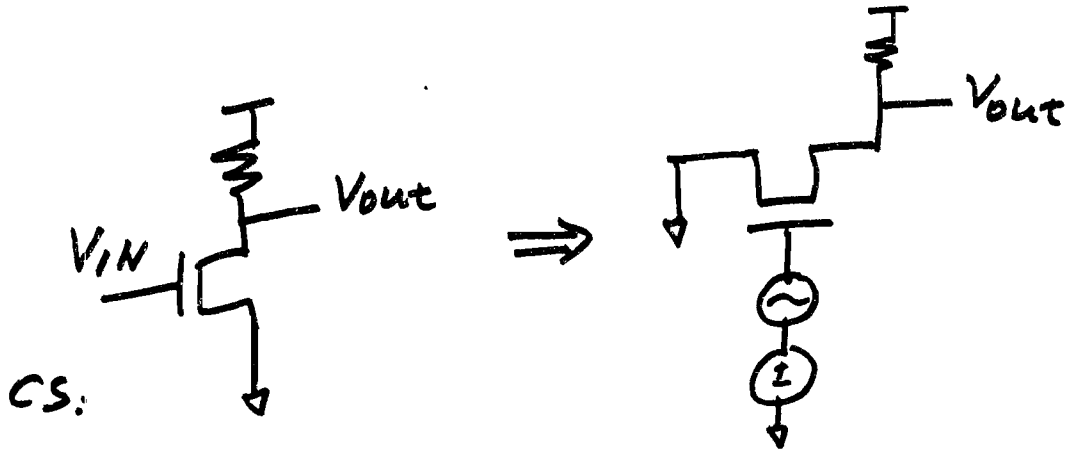


non-inverting

Your DC analysis the same!

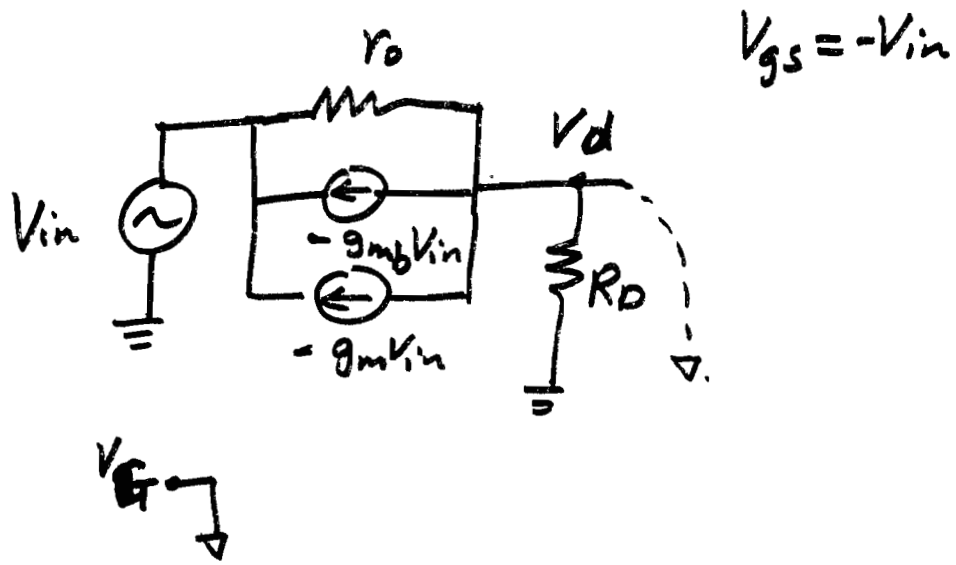Small signal analysis: \rightarrow body effect!




$G_m = ?$

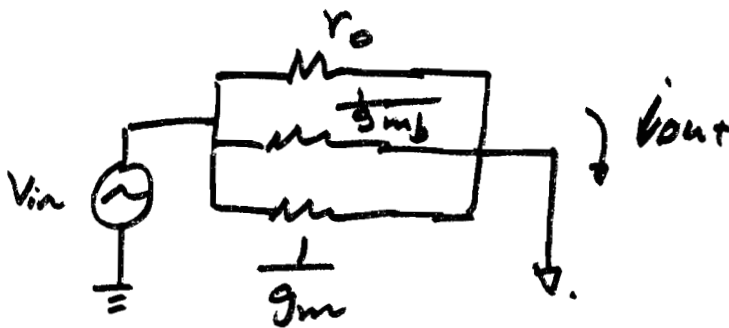

$$G_m = \frac{i_{out}}{V_{in}} = r_o \parallel \frac{1}{g_m} \parallel \frac{1}{g_m} = \frac{1}{r_o} + g_m(1+x)$$

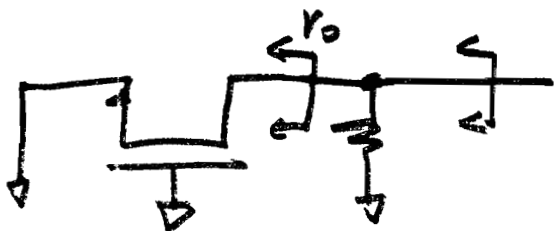Here is ^{the} Rare case where g_m help G_m .



$$R_{out} = r_o \parallel R_D$$

$$A_v = G_m R_{out} = g_m(1+x) (r_o \parallel R_D)$$

Same as CS.

What is Rin ?

$$i_t + \frac{V_e - V_{out}}{r_o} g_m (1+\alpha) V_e = 0$$

$$V_{out} = i_t R_D$$


$$\frac{V_e}{i_t} = R_{in} = \frac{r_o + R_D}{(1+\alpha) g_m r_o}$$

↙ too small.




$$R_{in} = \frac{r_o + R_D}{(1+\alpha) g_m r_o}$$

- ★ $\left\{ \begin{array}{l} R_D < r_o \\ R_D = r_o \\ R_D > r_o \end{array} \right. \quad \begin{array}{l} R_{in} \doteq \frac{1}{g_m} \quad (100 \Omega) \\ R_{in} \doteq \frac{2}{g_m} \\ R_{in} \doteq \frac{R_D}{(1+\alpha) g_m r_o} \end{array}$

Common Gate with R_s

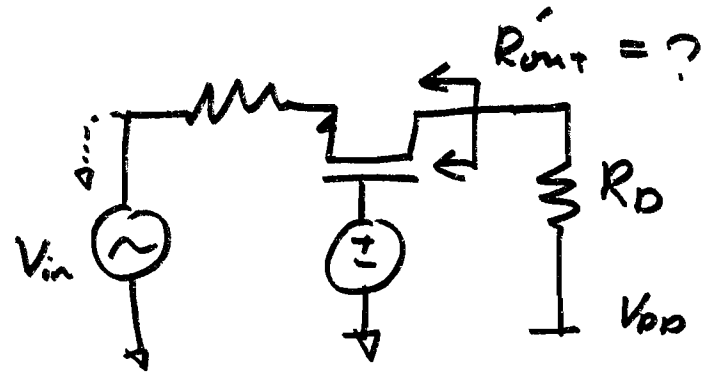

exactly as CS!

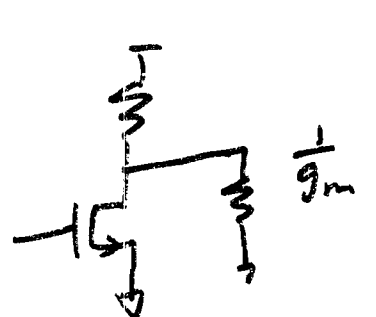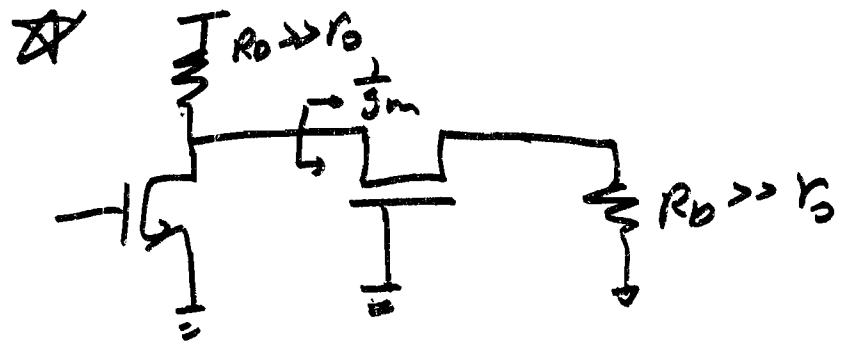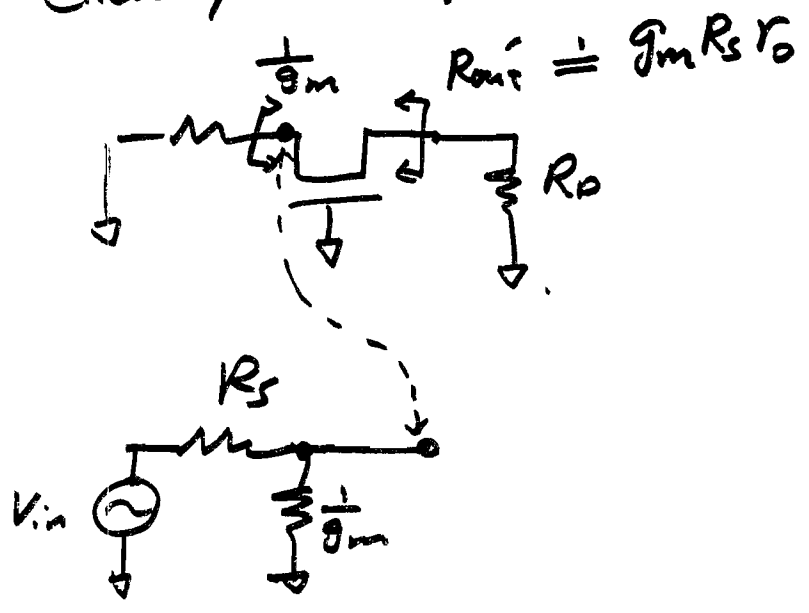

$$R_{out} = \frac{1}{g_m} \quad G_m = -g_m$$

$$A_{V_1} = -g_m \cdot R_{out} = -1$$

$$A_{V_2} = g_m r_o$$