

summary sheet

pg 8

$$g_m = \sqrt{2k' \frac{W}{L} I_{D_S}}$$

$$V_{D_{SAT}} = \left(\frac{2I_{D_S}}{k' \frac{W}{L}} \right)^{\frac{1}{2}}$$

$$r_o = \frac{1}{\lambda I_{D_S}}$$

$$\chi = \frac{\gamma}{\sqrt{2(2\phi_f + V_{SB})}}$$


$$g_{mb} = \chi g_m$$

$$V_{T_i} = V_{T_0} + \gamma \left(\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f} \right)$$

Summary sheet (small signal)

P1

two port.

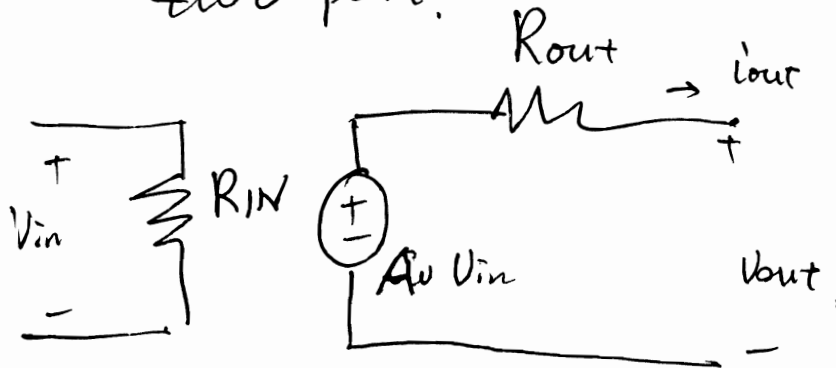

$$R_{in} = \frac{V_{in}}{i_{in}} \Big|_{i_{out}=0} \text{ (open at output)}$$


$$R_{out} = \frac{V_{out}}{(-i_{out})} \Big|_{V_{in}=0} \text{ (short input)}$$

$$G_m = \frac{i_{out}}{V_{in}} \Big|_{V_{out}=0} \text{ (short at output)}$$

$$A_v = G_m R_{out}$$

Summary Sheet (small signal)

P2.

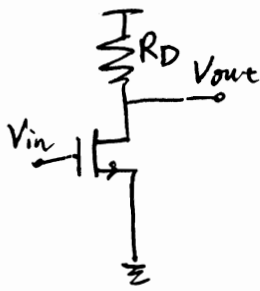

CS config.

$$G_m = -g_m$$


$$R_{out} = R_D \parallel r_o$$

$$R_{in} = \infty$$

$$A_v = R_m R_{out} = -g_m (R_D \parallel r_o)$$

High gain: $A_v = 100 \sim 1000$

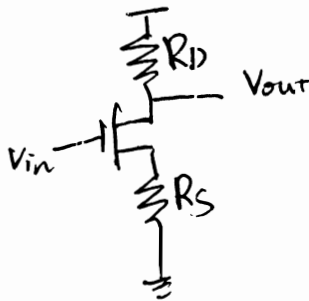
Moderate R_{out} : 10s of $k\Omega$
or $k\Omega$



CS config.
with source degeneration.

$$R_{out} = \left\{ R_S + r_o [1 + g_m (1 + \chi) R_S] \right\} \parallel R_D$$
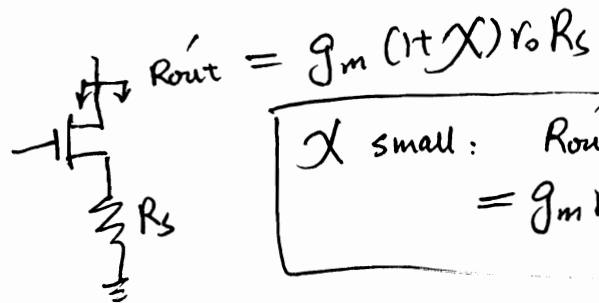
$$\approx g_m (1 + \chi) r_o R_S \parallel R_D$$




$$\chi \text{ small: } R_{out} = g_m r_o R_S$$

$$R_{in} = \infty$$

$$G_m = \frac{-g_m}{1 + g_m (1 + \chi) R_S} \stackrel{\substack{\downarrow \text{if body effect} \\ \text{small}}}{\approx} \frac{-g_m}{1 + g_m R_S}$$

$$A_v = G_m R_{out} \approx -\frac{R_D}{R_S}$$

CG config.

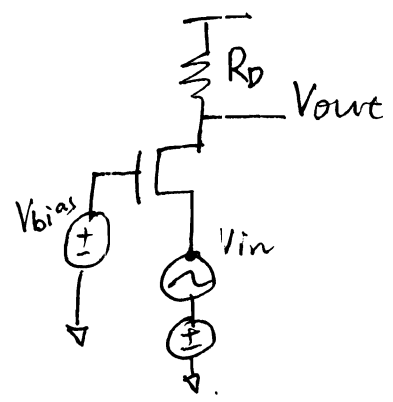

DC analysis is the same as CS.


$$R_{out} = r_o \parallel R_D$$

$$R_{in} = \begin{cases} \frac{1}{g_m} & R_D < r_o \\ \frac{2}{g_m} & R_D = r_o \\ \frac{R_D + r_o}{(1+\chi) g_m r_o + 1} & R_D > r_o \end{cases}$$

$$G_m = g_m (1+\chi)$$

$$A_v = g_m (1+\chi) (r_o \parallel R_D)$$

CG with R_S

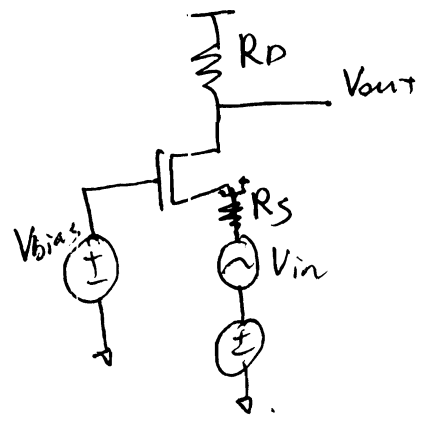


$$R_{out} = g_m (1+\chi) R_S \parallel R_D$$

$$G_m = \frac{(1+\chi) g_m}{1 + (1+\chi) g_m R_S}$$

$$R_{in} = R_S + \begin{cases} \frac{1}{g_m} & R_D < r_o \\ \frac{2}{g_m} & R_D = r_o \\ \frac{R_D + r_o}{(1+\chi) g_m r_o + 1} & R_D > r_o \end{cases}$$

$$A_v = G_m R_{out}$$

CD (source follower)

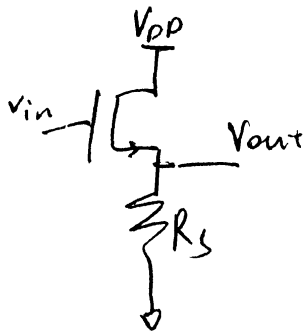


$$R_{out} = \frac{1}{(1+\alpha)g_m} \parallel R_S \rightarrow \text{low} \rightarrow 10 \sim 1K\Omega$$

$$R_{in} = \infty$$



$G_m =$ very low.

$$A_v = \frac{g_m R_S}{(1+\alpha)g_m R_S + 1} \approx 1 \quad \text{unit gain.}$$

resistor equivalent.

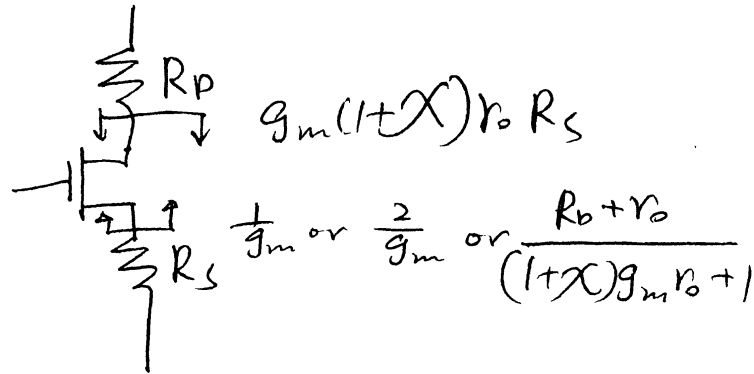

Problem 1:

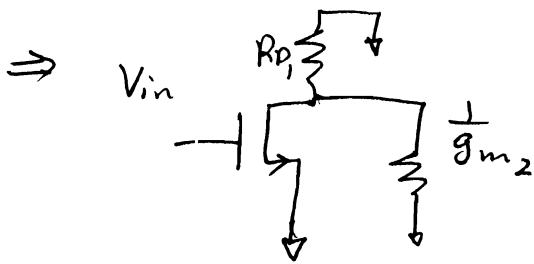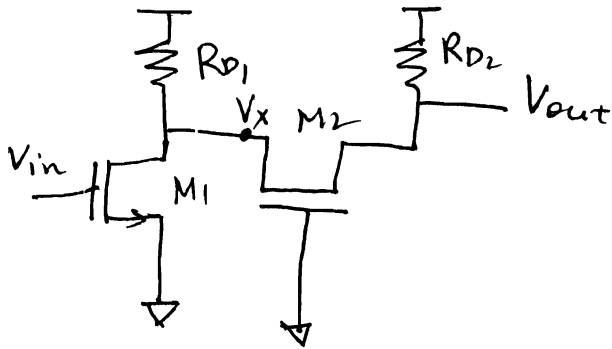

$$\frac{V_x}{V_{in}} = A_{v1} = -g_{m1} \left(\frac{1}{g_{m2}} \parallel R_{D1} \right)$$

$$R_{D1}, r_{o1} \gg \frac{1}{g_{m2}}$$

$$\Rightarrow A_{v1} = -g_{m1} \cdot \frac{1}{g_{m2}}$$

$$\text{if } g_{m1} = g_{m2} \quad A_{v1} = -1$$

$$A_{v2} = ?$$

$$A_{v2} = g_{m2} (1 + X) (r_{o2} \parallel R_{D2})$$


$$\text{if } R_{D2} \gg r_{o2} \quad X \rightarrow 0$$

$$\Rightarrow A_{v2} = g_{m2} r_{o2}$$


$$\Rightarrow A_v = A_{v1} \cdot A_{v2} = -g_{m2} r_{o2}$$

$$\text{if } R_{D2} \ll r_{o2}, \quad X \rightarrow 0 \quad A_v = -g_{m2} R_{D2} = -g_m R_{D2}$$

problem 2.

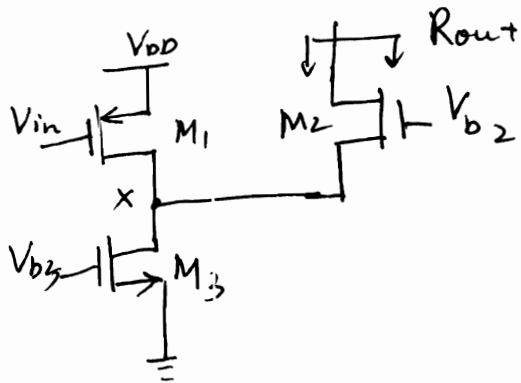


$$R_x = r_{o1} \parallel r_{o3}$$

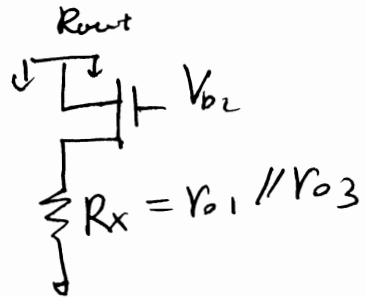

$$R_{out} = g_{m2} (1 + \chi) r_{o2} R_x$$
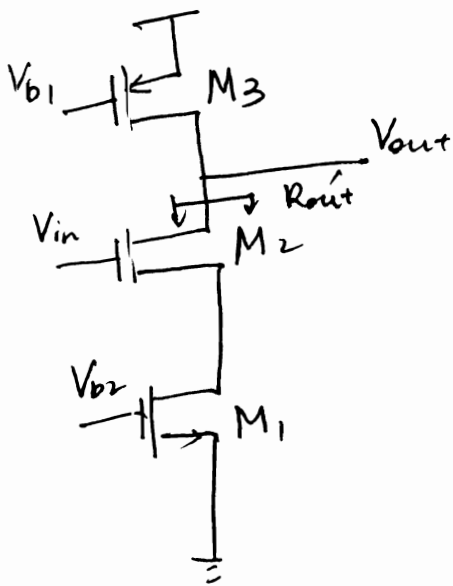
$$= g_{m2} (1 + \chi) r_{o2} (r_{o1} \parallel r_{o3})$$



$$R_{out} = R_{out}' \parallel r_{o3}$$

$$R_{out}' = g_{m2} (1 + \chi) r_{o2} r_{o1}$$