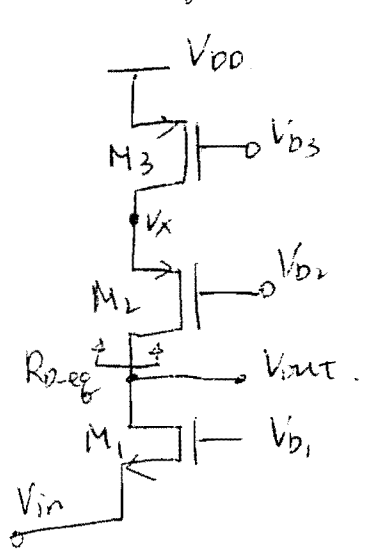


5.21

a) $\lambda = 0$, no body effect.



M_1 is common gate (without R_s)

$$A_v = \frac{(g_{m1} r_{o1} + 1) R_D}{r_{o1} + R_D}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{(g_{m1} r_{o1} + 1) R_{D,eq}}{r_{o1} + R_{D,eq}}$$

$$R_{D,eq} = r_{o2} + (1 + g_{m2} r_{o2}) r_{o3}$$

$$\text{So } A_v = \frac{(1 + g_{m1} r_{o1}) (r_{o2} + (1 + g_{m2} r_{o2}) r_{o3})}{r_{o1} + r_{o2} + (1 + g_{m2} r_{o2}) r_{o3}}$$

by KCL, KVL.


$$\textcircled{1} \quad -\frac{V_x}{r_{o3}} = g_{m2} V_x + \frac{V_x - V_{out}}{r_{o2}} = \frac{V_{out} - V_{in}}{r_{o1}} - g_{m1} V_{in} \quad \textcircled{3}$$

$$\textcircled{1}, \textcircled{2} \rightarrow V_x = \frac{V_{out}}{1 + r_{o2} (g_{m2} + \frac{1}{r_{o3}})}$$

$$\textcircled{1}, \textcircled{3} \rightarrow \frac{V_{out} - V_{in}}{r_{o1}} - g_{m1} V_{in} = -\frac{V_{out}}{r_{o3} + r_{o2} (1 + g_{m2} r_{o3})}$$



$$A_v = \frac{V_{out}}{V_{in}} = \frac{(1 + g_{m1} r_{o1}) (r_{o3} + (1 + g_{m2} r_{o3}) r_{o2})}{r_{o1} + r_{o3} + r_{o2} (1 + g_{m2} r_{o3})}$$

b) $\bar{\gamma} = 0$ No Body effect.

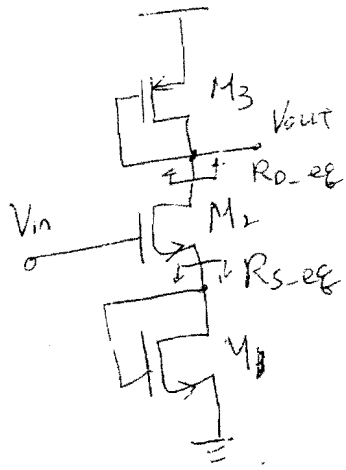

M_2 : CS with source degeneration.
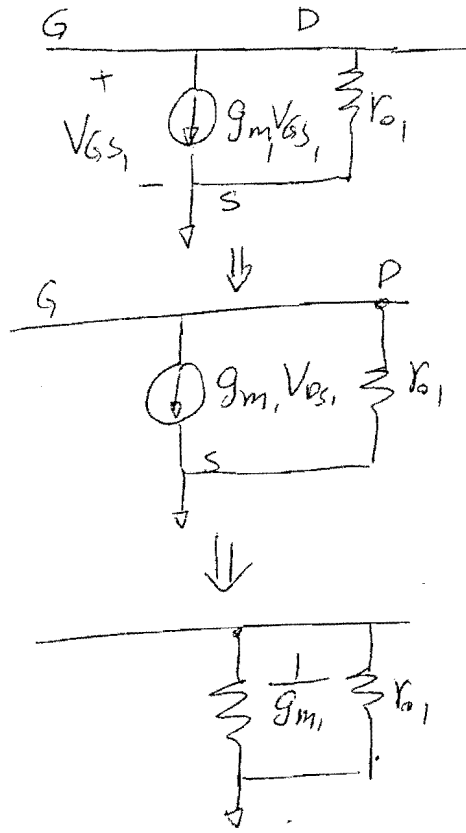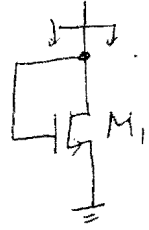
$$G_m = \frac{g_{m2} r_{o2}}{R_s + (1 + g_{m2} R_s) r_{o2}}$$



$V_{gs1} = V_{out}$

$R_{s-eg} = \frac{1}{g_{m1}} \parallel r_{o1}$

$\Rightarrow R_{o-eg} = \frac{1}{g_{m3}} \parallel r_{o3}$

$R_{s-eg} = \frac{1}{g_{m1}} \parallel r_{o1}$


$$G_m = \frac{g_{m2} r_{o2}}{\left(\frac{1}{g_{m1}} \parallel r_{o1}\right) + (1 + g_{m2} \left(\frac{1}{g_{m1}} \parallel r_{o1}\right)) r_{o2}}$$

$R_{out} = R_{o-eg} \parallel \left\{ (1 + g_{m2} R_{s-eg}) r_{o2} + R_{s-eg} \right\}$

③

$$R_{out} = \left(\frac{1}{g_{m3}} \parallel r_{o3} \right) \parallel \left\{ \left[1 + g_{m2} \left(\frac{1}{g_{m1}} \parallel r_{o1} \right) \right] r_{o2} + \left(\frac{1}{g_{m1}} \parallel r_{o1} \right) \right\}$$

$$A_v = -G_m R_{out} = \dots$$

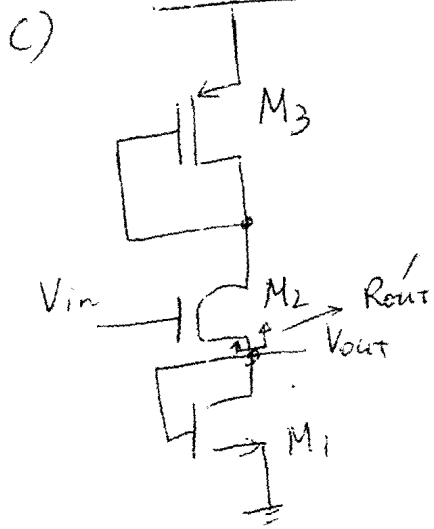

M_2 is common drain with R_{s-eg} , R_{d-eg} .

$$R_{s-eg} = \frac{1}{g_{m1}} \parallel r_{o1}$$


$$R_{d-eg} = \frac{1}{g_{m3}} \parallel r_{o3}$$

$$A_v = \frac{R_{s-eg}}{R_{s-eg} + R_{out}'}$$

$$R_{out}' = \frac{R_{d-eg} + r_{o2}}{1 + g_{m2} r_{o2}}$$

$$\Rightarrow A_v = \frac{\frac{1}{g_{m1}} \parallel r_{o1}}{\frac{1}{g_{m1}} \parallel r_{o1} + \frac{\frac{1}{g_{m3}} \parallel r_{o3} + r_{o2}}{1 + g_{m2} r_{o2}}}$$

M₂ CS with source degeneration (4)

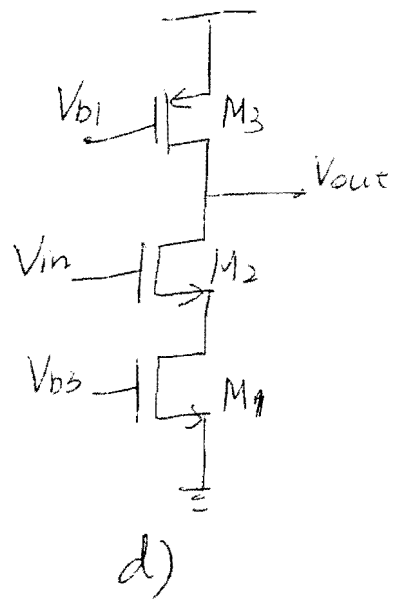


$$G_m = \frac{g_{m2} r_{o2}}{R_{s,eq} + (1 + g_{m2} R_{s,eq}) r_{o1}}$$

$$= \frac{g_{m2} r_{o2}}{r_{o1} + (1 + g_{m2} r_{o1}) r_{o2}}$$

$$R_{out} = r_{o3} \parallel [(1 + g_{m2} r_{o1}) r_{o2} + r_{o1}]$$

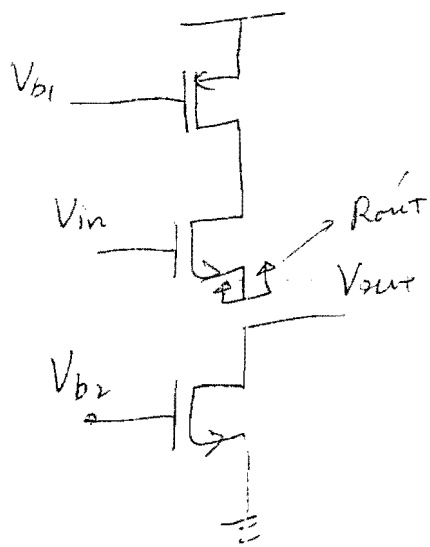
$$A_v = \frac{V_{out}}{V_{in}} = -G_m R_{out} = -\frac{g_{m2} r_{o2} r_{o3}}{r_{o3} + (1 + g_{m2} r_{o1}) r_{o2} + r_{o1}}$$



$$R_{out}' = \frac{r_{o3} + r_{o2}}{1 + g_{m2} r_{o2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{r_{o1}}{r_{o1} + R_{out}'} = \frac{r_{o1} (1 + g_{m2} r_{o2})}{r_{o1} (1 + g_{m2} r_{o2}) + r_{o2} + r_{o3}}$$

(e)

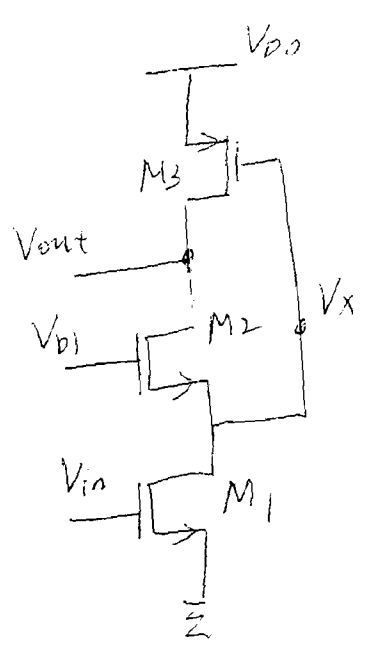

$$\textcircled{1} \quad -\left(\frac{V_{DD}}{r_{o3}} + g_{m3} V_x\right) = \textcircled{2} \left(\frac{V_{out} - V_x}{r_{o2}} - g_{m2} V_x\right)$$

$$= \frac{V_x}{r_{o1}} + g_{m1} V_{in} \quad \textcircled{3}$$

$$\textcircled{1}, \textcircled{2} \rightarrow \frac{V_x}{r_{o2}} + g_{m2} V_x - g_{m3} V_x = \frac{V_{out}}{r_{o2}} + \frac{V_{out}}{r_{o3}}$$

$$\rightarrow V_x = \frac{\frac{1}{r_{o2}} + \frac{1}{r_{o3}}}{\frac{1}{r_{o2}} + g_{m2} - g_{m3}} V_{out}$$


$$\textcircled{1}, \textcircled{3} \quad -\frac{V_{out}}{r_{o3}} = g_{m3} V_x = \frac{V_x}{r_{o1}} + g_{m1} V_{in}$$

$$-\frac{V_{out}}{r_{o3}} - \left(g_{m3} + \frac{1}{r_{o1}}\right) \frac{\frac{1}{r_{o2}} + \frac{1}{r_{o3}}}{\frac{1}{r_{o2}} + g_{m2} - g_{m3}} V_{out} = g_{m1} V_{in}$$

⇒

$$-V_{out} \left[\frac{1}{r_{o3}} + \frac{(1+g_{m3}r_{o1})(r_{o3}+r_{o2})}{r_{o1}r_{o3}[1+(g_{m2}-g_{m3})r_{o2}]} \right] = g_{m1} \cdot V_{in}$$
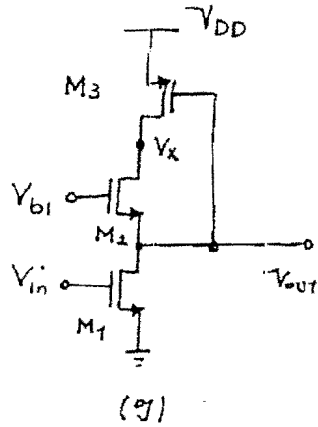
$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1} r_{o1} r_{o3} [1+(g_{m2}-g_{m3})r_{o2}]}{r_{o1} [1+(g_{m2}-g_{m3})r_{o2}] + (1+g_{m3} \cdot r_{o1})(r_{o3}+r_{o2})}$$




$$V_x = \frac{\frac{1}{r_{o2}} + g_{m2} - g_{m3}}{\frac{1}{r_{o2}} + \frac{1}{r_{o3}}} \cdot V_{out}$$

$$-\frac{V_x}{r_{o3}} - g_{m3} V_{out} = \frac{V_{out}}{r_{o1}} + g_{m1} \cdot V_{in}$$

$$-\frac{\frac{1}{r_{o2}} + g_{m2} - g_{m3}}{\frac{r_{o3}}{r_{o2}} + 1} V_{out} - g_{m3} V_{out} = \frac{V_{out}}{r_{o1}} + g_{m1} V_{in}$$

$$-V_{out} \left[\frac{1+(g_{m2}-g_{m3})r_{o2}}{r_{o3}+r_{o2}} + g_{m3} + \frac{1}{r_{o1}} \right] = g_{m1} V_{in}$$
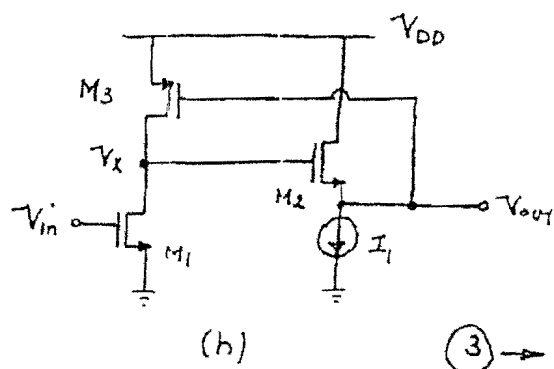
$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1} r_{o1} (r_{o2}+r_{o3})}{r_{o1} [1+(g_{m2}-g_{m3})r_{o2}] + (r_{o2}+r_{o3})(1+g_{m3} \cdot r_{o1})}$$



$$\textcircled{1} \quad - \left(\frac{V_x}{r_{o3}} + g_{m3} V_{out} \right) = g_{m1} V_{in} + \frac{V_x}{r_{o1}} \quad \textcircled{2}$$

$$-\frac{V_{out}}{r_{o2}} + g_{m2} (V_x - V_{out}) = 0 \quad \textcircled{3} \quad \text{@ output node}$$

$$\textcircled{3} \rightarrow V_x = \frac{\frac{1}{r_{o2}} + g_{m2}}{g_{m2}} \cdot V_{out} = \frac{1+g_{m2}r_{o2}}{g_{m2}r_{o2}} V_{out}$$

$$\textcircled{1}, \textcircled{2} \rightarrow - \left[\left(\frac{1}{r_{o3}} + \frac{1}{r_{o1}} \right) \frac{1+g_{m2} \cdot r_{o2}}{g_{m2} \cdot r_{o2}} + g_{m3} \right] V_{out} = g_{m1} \cdot V_{in}$$

$$\frac{V_{out}}{V_{in}} = - \frac{g_{m1} \cdot g_{m2} r_{o1} r_{o2} r_{o3}}{(r_{o1}+r_{o3})(1+g_{m2} \cdot r_{o2}) + g_{m2} g_{m3} r_{o1} r_{o2} r_{o3}}$$

Dr Wang's cheat sheet.

$$V_{th} = V_{th0} + \gamma (\sqrt{2\phi_f + V_{SB}} - \sqrt{2\phi_f})$$


$$V_{DSAT} = \left(\frac{2I_{DS}}{k' \frac{W}{L}} \right)^{\frac{1}{2}}$$

$$\chi = \frac{\gamma}{\sqrt{2(2\phi_f + V_{SB})}}$$

$$r_o = \frac{1}{\lambda I_{DS}}$$

$$g_m = \sqrt{2k' \frac{W}{L} I_{DS}}$$

$$g_{mb} = \chi g_m$$

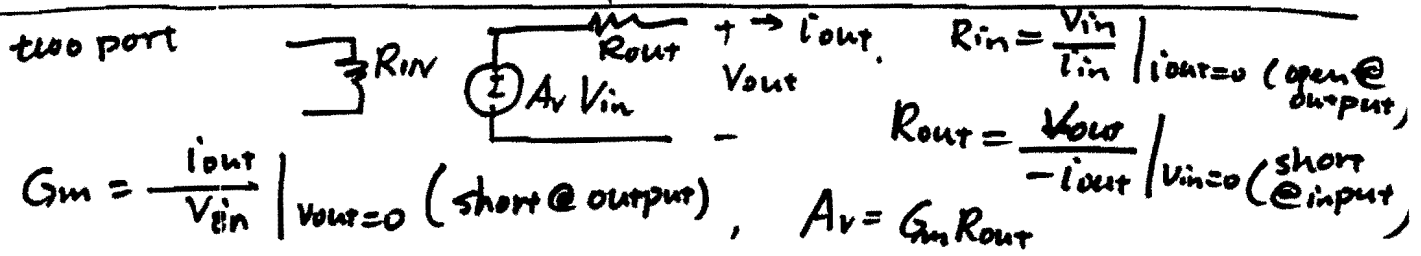

CS with R_s Accurate No Body effect

$G_m = \frac{-g_m r_o}{R_s + (1 + g_m R_s) r_o}$ $R_{in} = \infty$
 $R_{out} = R_D \parallel ((1 + g_m R_s) r_o + R_s)$
 $A_v = G_m R_{out}$
If Body effect: $g_m (1 + \chi)$

Approximate

$g_m R_s \gg 1, R_s \ll r_o$
 $G_m \approx \frac{-g_m}{1 + g_m R_s}$ if $R_s = 0$ High Gain
 $R_{out} \approx R_D \parallel g_m r_o R_s = R_D$
 $A_v \approx -\frac{R_D}{R_s}, R_{in} = \infty$

CG with R_s Accurate

$R_{in} = \frac{R_D + r_o}{g_m r_o + 1}$
 $R_{out}' = (1 + g_m r_o) R_s + r_o = R_s + (1 + g_m R_s) r_o$
 $R_{out} = R_{out}' \parallel R_D$
 $G_m = \frac{(1 + g_m r_o) R_D}{(r_o + R_D) [(1 + g_m r_o) R_s + r_o]}$
 $A_v = \frac{(g_m r_o + 1) R_D}{r_o + R_D}$

$R_{in} = \begin{cases} \frac{1}{g_m} & r_o \gg R_s \\ \frac{2}{g_m} & r_o = R_D \\ \text{Same } R_D \gg r_o & \text{as accurate} \end{cases}$
 $R_{out} \approx g_m r_o R_s \parallel R_D$
 $G_m \approx g_m \quad R_s \rightarrow 0$
 $A_v \approx g_m (r_o \parallel R_D)$ $R_s \rightarrow 0$

CD with R_D

$R_{in} = \infty$
 $R_{out}' = R_D \parallel R_s$ $G_m = \text{too long!}$
 $R_{out} = \frac{R_D + r_o}{1 + g_m r_o}$
 $A_v = \frac{V_{out}}{V_{in}} = \frac{R_s}{R_s + R_{out}'}$
 $A_v = \frac{R_s}{R_s}$

$R_{in} = \infty$
 $R_{out}' \approx \frac{1}{g_m}, R_{out} = \frac{1}{g_m} \parallel R_s$
 $G_m = \text{too long!}$
 $A_v \approx \frac{g_m R_s}{g_m R_s + 1} \approx 1$
 small R_{out} , unit gain