

# Problem Practice 2


## Differential Pairs and Current Sources


**Problem 1.** A) What is  $R_{REF}$  So that  $I_{DS\_M6} = 10\mu A$  ?

B) What is the Maximum Voltage Swing at the  $V_{out}$  ?

C) What is the output resistance ?

D) What is the gain ?

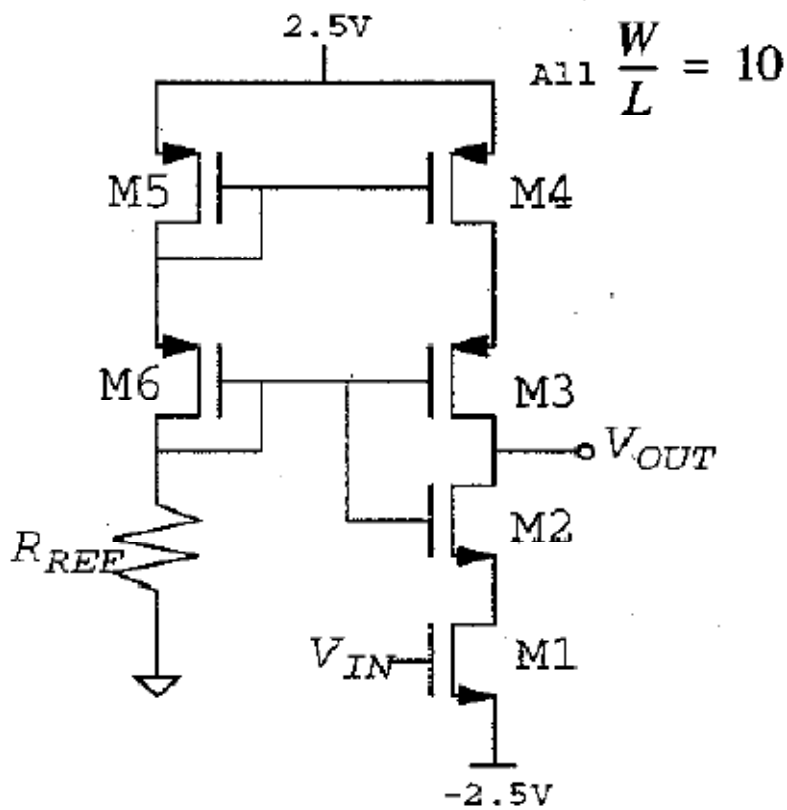

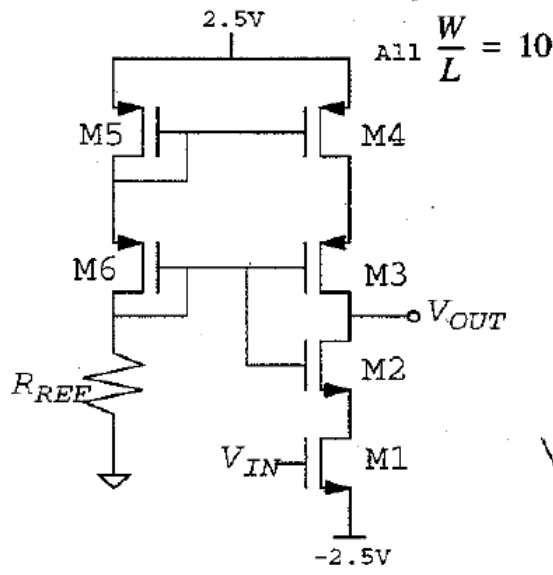

$$V_{DSAT5} = \left( \frac{2I_D}{\mu W/L} \right)^{1/2}$$

$$= \left( \frac{2 \cdot 10 \times 10^{-6}}{10^{-4} \cdot 10} \right)^{1/2} = 0.14$$

a) What is  $R_{REF}$  so that  $I_{DS} = 10 \mu A$ ?

$R_{REF} = 122 \text{ k}\Omega$

$$V_{G6} = V_{DD} - 2(V_T + V_{DSAT}) = 2.5 - 2(0.5 + 0.14) = 1.22 \text{ V}$$

$$R_{REF} = \frac{V_{G6}}{I} = \frac{1.22}{10 \mu A} = 122 \text{ k}\Omega$$

b) What is the maximum swing at

$V_{OUT}$  which has high gain?

$V_{OUT, MAX} = 1.72 \text{ V}, V_{OUT, MIN} = 0.72 \text{ V}$

$$V_{OUT, MAX} = V_{DD} - (V_T + V_{DSAT}) - V_{DSAT}$$

$$= 2.5 - (0.5 + 0.14) - 0.14 = 1.72 \text{ V}$$

$$V_{OUT, MIN} = V_{G6} - V_T = 1.22 - 0.5 = 0.72 \text{ V}$$

c) what is the output resistance?

$$R_{OUT} = 76 \Omega$$

$$r_D = \frac{1}{\lambda I_D} = 10 \text{ M}\Omega$$

$$g_m = \frac{2 I_D}{V_{DSAT}} = 141 \frac{\mu\text{A}}{\text{V}}$$

$$R_{OUT} = r_{O1} \parallel r_{O2} \approx r_{O3} r_{O4} g_{m3} \parallel g_{m2} r_{O2} r_{O1} \\ \approx \frac{141 \text{ G}\Omega}{2} = 76 \Omega$$

d) What is the gain?  $10^6$


$$G_m = -(1+\lambda) g_m = -g_m$$

$$A_v = -g_m r_{out} = 141 \mu\text{A/V} \cdot 76 \Omega \\ = 10^6$$

Problem 2 1) If  $V_{IN+} = V_{IN-} = V_{IN}$ , what is  $V_s/V_{IN}$  ?


2) If  $V_{IN+} = 0\text{V}$  and  $V_{IN-} = V_{IN}$ , what is  $V_s/V_{IN}$  ?

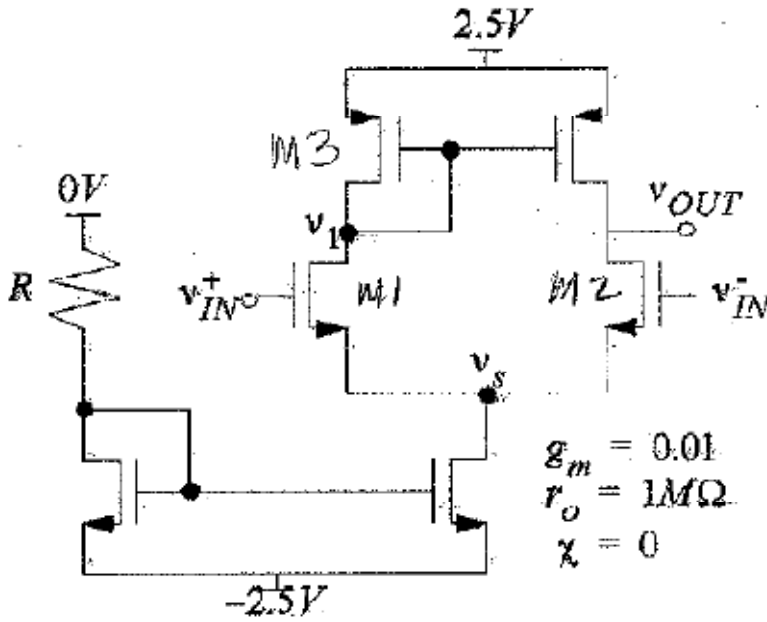3) If  $V_{IN+} = V_{IN}/2$  and  $V_{IN-} = -V_{IN}/2$ , What is  $V_1/V_{IN}$  ?



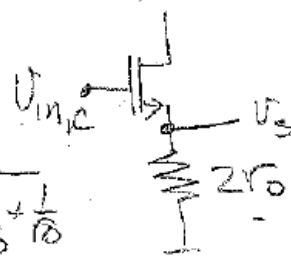
a) If  $v_{IN}^+ = v_{IN}^- = v_{IN}$ , what is  $v_S/v_{IN}$ ? 1

$$\frac{v_S}{v_{IN}} = \frac{g_m}{g_m(1+\chi) + \frac{1}{R_S} + \frac{1}{2r_o}} = \frac{.01}{.01 + \frac{1}{2r_o} + \frac{1}{r_o}} \approx 1$$



b) If  $v_{IN}^+ = 0V$  and  $v_{IN}^- = v_{IN}$ , what is  $v_S/v_{IN}$ ? .33

$$G_m R_{out} = 0.33$$

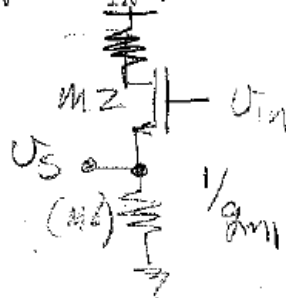


$$G_m = g_m$$

$$R_{out} = r_o || \frac{1}{g_m1} || \frac{2}{g_m2}$$


$$= \frac{0.33}{g_m}$$

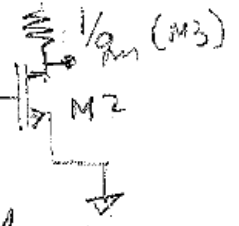c) If  $v_{IN}^+ = +v_{IN}/2$  and  $v_{IN}^- = -v_{IN}/2$ , what is  $v_1/v_{IN}$ ? -1

$$\frac{v_1}{v_{IN}} = -g_m R_{out} = -\frac{1}{g_m} \left( \frac{1}{r_o} \right) = -1$$



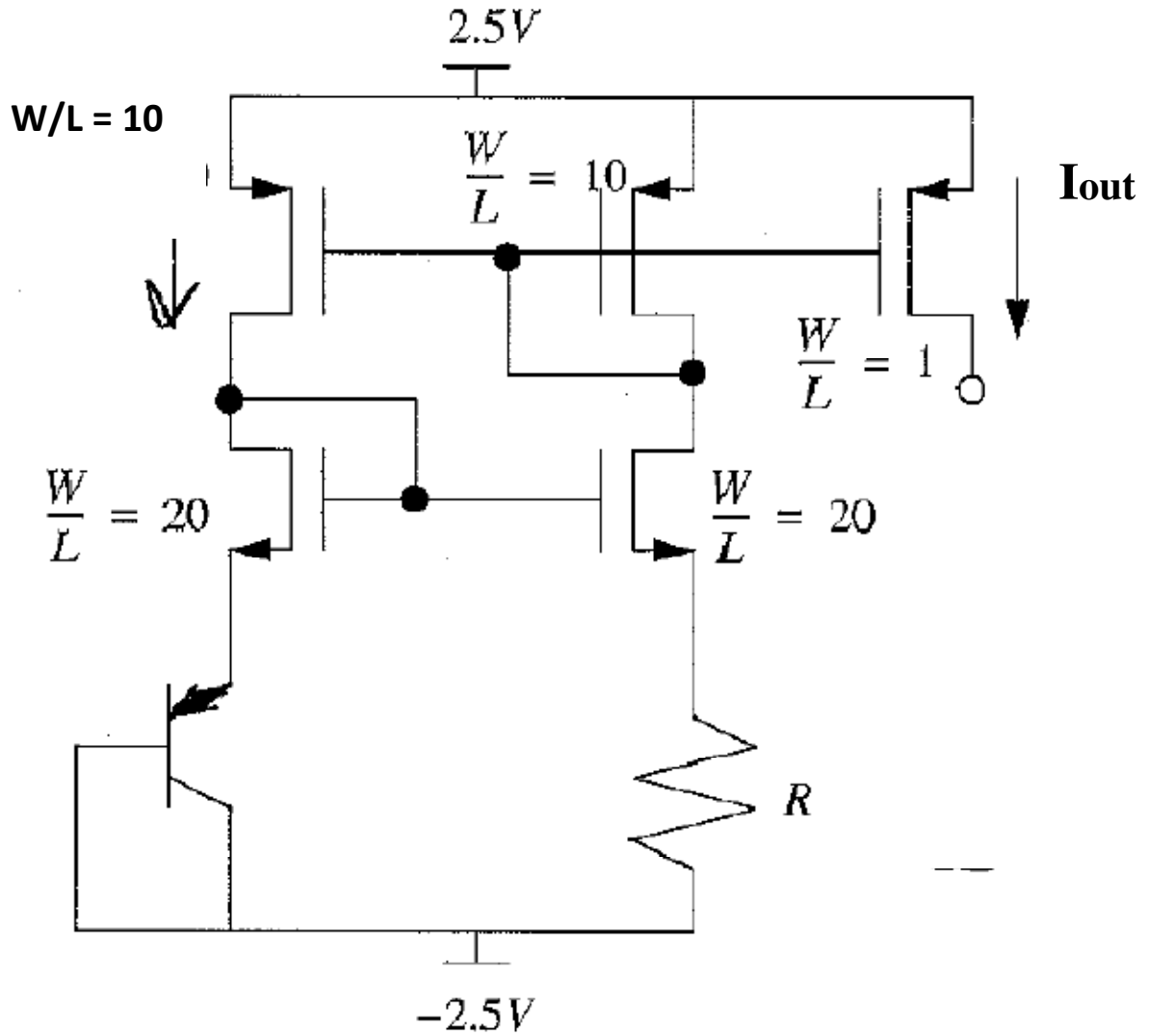**Problem 3** What is the value of  $R$  so that  $I_{out} = 100\mu A$  ?



What is the value of R so that

$I_{OUT} = 100\mu A$ ?  $R = \underline{500\Omega}$

$$R = \frac{V_{EB(ON)}}{(100\mu A)10} = \frac{.5}{.01 \times 10^{-4} \times 10} = 500\Omega$$


$$I_Q = -\frac{V_1}{R} = \frac{\mu'}{2} (V_1 - (-2.5) - V_T)^2$$

$$= \frac{\mu'}{2} (V_1 + 2)^2$$

$$V_1^2 + 24V_1 + 4 = 0 \quad V_1 = -.17V,$$

$$I_Q = .17mA$$

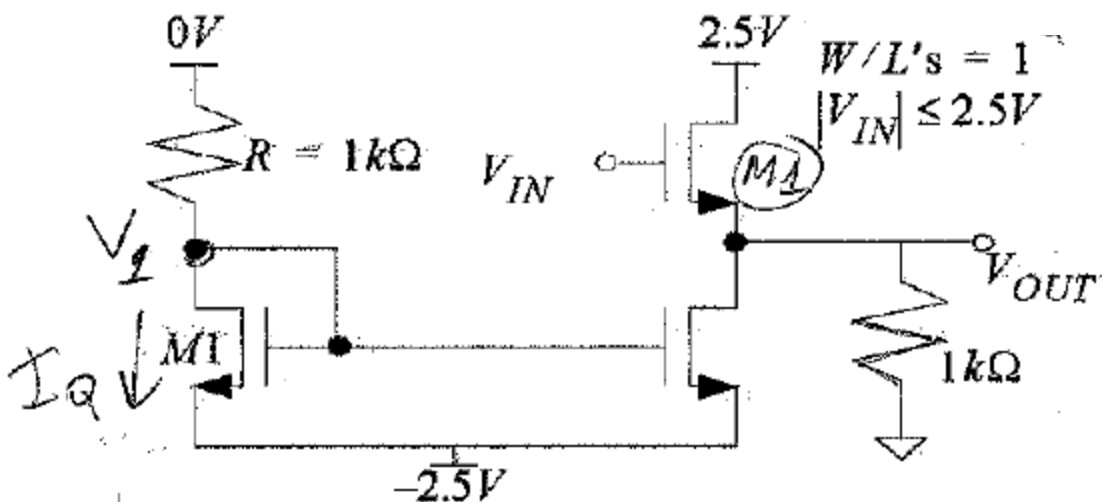Problem 4. What is  $V_{out,max}$ ? What is  $V_{out,min}$ ? If R is chosen so that current through M1 is 0.1mA, what is the efficiency of this circuit assuming the output must be centered around 0V?



a) What is the most positive voltage that  $V_{OUT}$  can achieve? .027 Volts

$$V_{OUT,MAX} = V_{DD} - V_T - V_{DSAT,1} = 2 - \left[ \frac{2(I_Q + \frac{V_{OUT}}{1k})}{k'W/L} \right]^{1/2}$$

$$(2 - V_{OUT,MAX})^2 = \frac{2(I_Q + \frac{V_{OUT}}{1k})}{k'W/L} ; V_{OUT,MAX}^2 - 2.4V_{OUT,MAX} + 1.64 = 0$$

$$V_{OUT,MAX} = \underline{\underline{.027V}}$$

b) What is the most negative voltage that  $V_{OUT}$  can achieve? -.17V

$$V_{OUT,MIN} = -I_Q R_L = -(.17mA)(1k) = -.17V$$

c) If R is chosen so the current through  $M1$  is  $0.1mA$ , what is the efficiency of this circuit? Eff = 47%  
(Assume the output must be centered around 0V)

$$(2 - V_{OUT,MIN})^2 = \frac{2(1 \times 10^{-3} + 10^{-3} V_{OUT})}{10^{-4}}$$

$$V_{OUT,MAX}^2 - 2.4V_{OUT,MAX} + 2 = 0$$

$$V_{OUT,MAX} = \underline{\underline{.084V}}$$

$$P_{SUPPLY} = 3(25)(.1mA)$$

$$= .75mW$$

$$P_{LOAD} = \frac{V_{OUT,MAX}^2}{2R_L}$$

$$= \frac{(.084)^2}{2 \times 10^3}$$

$$= 3.5 \mu W$$