

Problem Practice 2


Differential Pairs and Current Sources

Problem 1. A) What is R_{REF} So that $I_{DS_M6} = 10\mu A$?

B) What is the Maximum Voltage Swing at the V_{out} ?

C) What is the output resistance ?


D) What is the gain ?

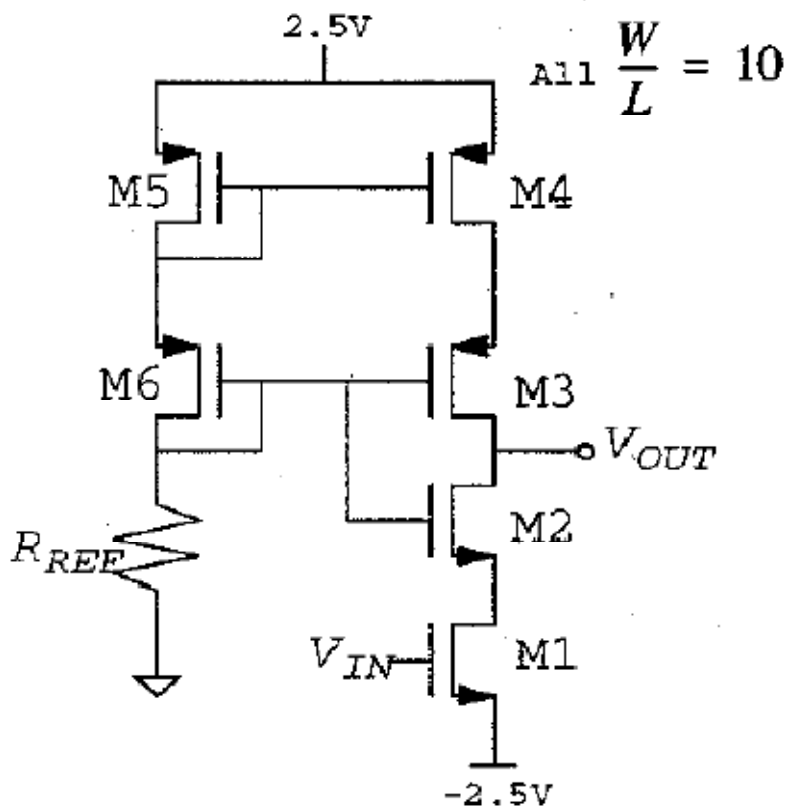


Problem 2 1) If $V_{IN+} = V_{IN-} = V_{IN}$, what is V_s/V_{IN} ?

2) If $V_{IN+} = 0V$ and $V_{IN-} = V_{IN}$, what is V_s/V_{IN} ?

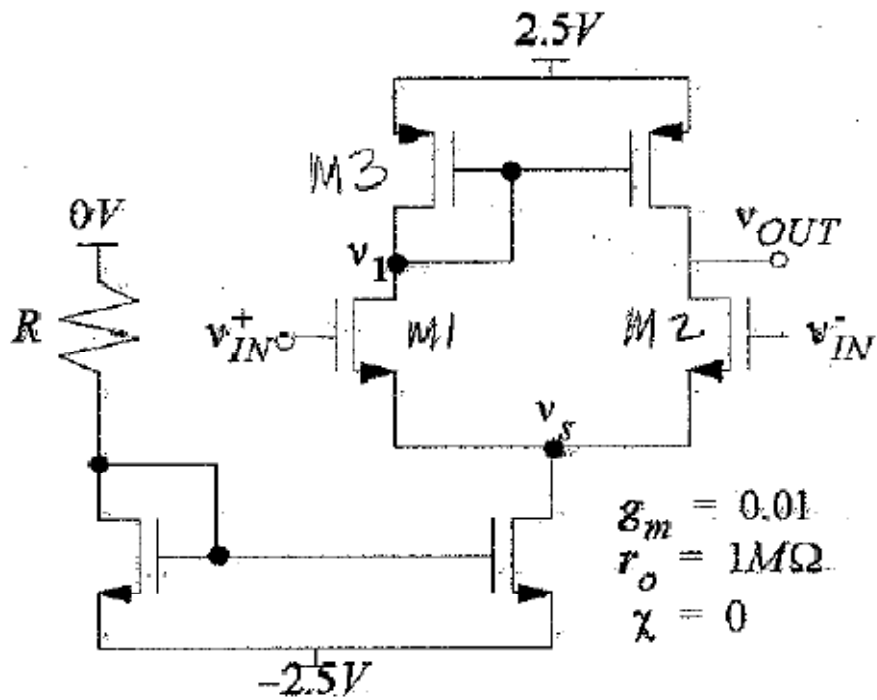3) If $V_{IN+} = V_{IN}/2$ and $V_{IN-} = -V_{IN}/2$, What is V_1/V_{IN} ?



Problem 3 What is the value of R so that $I_{out} = 100\mu A$?

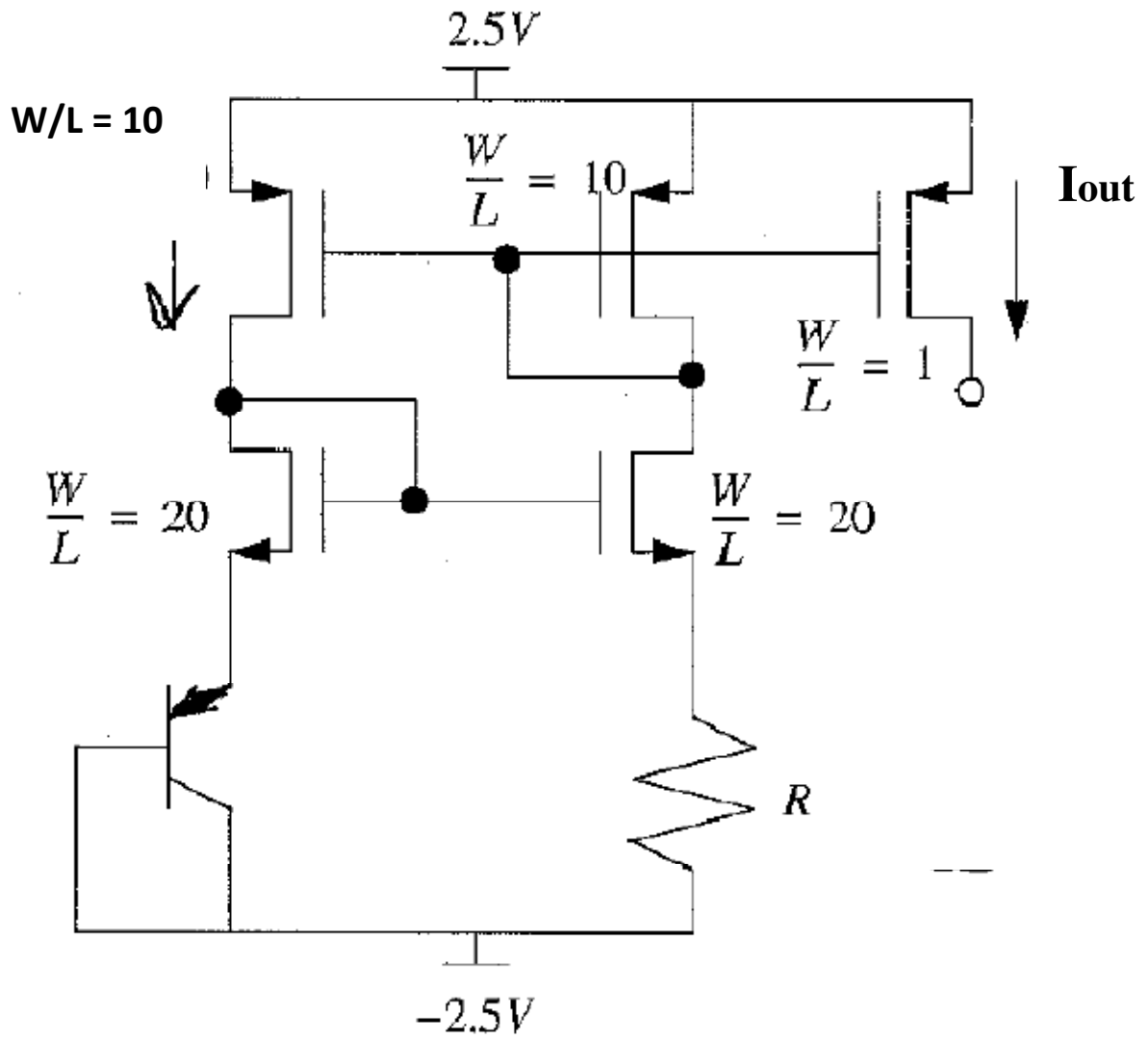

Problem 4. What is $V_{out,max}$? What is $V_{out,min}$? If R is chosen so that current through $M1$ is 0.1mA , what is the efficiency of this circuit assuming the output must be centered around 0V ?

