

In-class Exercise 1

(PAR 5)

- Create FSM to detect when four 1's have appeared on input stream (doesn't need to be consecutive)
 - input : w (bit)
 - output : f (bit)

- Create high-level FSM to achieve same functionality