

DC analysis

Objective: *Describe numerical methods, expose problems and discuss solution techniques*

Outline:

1. Problem formulation
2. Solution methods
3. Newton-Raphson scalar case
4. Multivariable Newton-Raphson method
5. Examples - exercises
6. Modifications to Newton-Raphson
7. DC convergence control in SPICE
8. Concluding remarks - suggestions,
9. Handling non-convergence cases.

Supplemental reading: Vladimirescu, The SPICE Book, Chapters: 4, 9.1 - 9.3, 10.3

1. Problem formulation

The mathematical form of circuit equations (MNA, traditional variables, Session. 3, sect. 3.3)

$$C(x) \frac{dx}{dt} + G(x)x = w .$$

Problem: for given, constant input, find selected circuit variables at equilibrium, i.e. when the time derivatives, $\frac{d}{dt}$, are ignored

$$G(x)x = w .$$

In the circuit terminology this means that for DC analysis the capacitors are open and the inductors are shorted.

DC analysis is a very fundamental function of all circuit simulators.

It is used in determining: operating point, initial conditions in transients, transfer curves etc.

Presence of nonlinear elements in the network makes the analysis very difficult.

Very often a simulator fails in DC analysis because of numerical complexity.

2. Solution methods

1. Newton - Raphson

(basic SPICE method)

2. Relaxation techniques

(Gauss-Seidel, Gauss-Jacobi)

3. Optimization procedures

4. Continuation techniques

- **inaccurate transient analysis (IBM ASTAP)**
- **source stepping (implemented as optional in some SPICE's)**

Alternative approaches

Reformulate problem:

$$G(x)x - w = f(x) = 0$$

Newton

$$\Gamma = \nabla f(x)$$

solve $\Gamma \delta = -f(x)$

substitute $x \leftarrow x + \delta$

and iterate.

The procedure has a local quadratic convergence.

Trust-region Newton's

same as Newton, with restriction $\|\delta_k\| \leq \Delta_k$

this is equivalent to solving $(\Gamma + \lambda I)\delta = -f(x)$, with some $\lambda \geq 0$.

Δ_k sufficiently small $\Rightarrow \delta$ decreases $\|f(x)\|$,

near solution $\lambda = 0$,

retains convergence properties.

Quasi-Newton: estimate Γ from $f(x_k), f(x_{k+1}), f(x_{k+2}), \dots$
can be incorporated in trust-region method.

3. Newton-Raphson scalar case

$$\mathbf{g}(\mathbf{y}^*) = \mathbf{0} \quad \mathbf{y}^* \text{ ---ideal (theoretical) solution.}$$

The iterative process is constructed for the increment, $\Delta\mathbf{y}$, defined as

$$\mathbf{y}^* = \mathbf{y}^{(k)} + \Delta\mathbf{y}$$

and is based on the linearization

$$\mathbf{g}(\mathbf{y}^{(k)} + \Delta\mathbf{y}) \cong \mathbf{g}(\mathbf{y}^{(k)}) + \mathbf{g}'(\mathbf{y}^{(k)})\Delta\mathbf{y}$$

where

$$\mathbf{g}' = \left. \frac{\partial \mathbf{g}}{\partial \mathbf{y}} \right|_{\mathbf{y}=\mathbf{y}^{(k)}} .$$

The increment is approximated as follows

$$\Delta\mathbf{y} = \mathbf{y}^* - \mathbf{y}^{(k)} \Rightarrow \Delta\mathbf{y} \cong \mathbf{y}^{(k+1)} - \mathbf{y}^{(k)}$$

which leads to the iterative equation


$$\mathbf{g}(\mathbf{y}^{(k)}) + \mathbf{g}'(\mathbf{y}^{(k)})(\mathbf{y}^{(k+1)} - \mathbf{y}^{(k)}) = \mathbf{0}$$

or else

$$g'(y^{(k)}) \cdot y^{(k+1)} = g'(y^{(k)}) \cdot y^{(k)} - g(y^{(k)})$$

$$k = 0, 1, 2, \dots$$

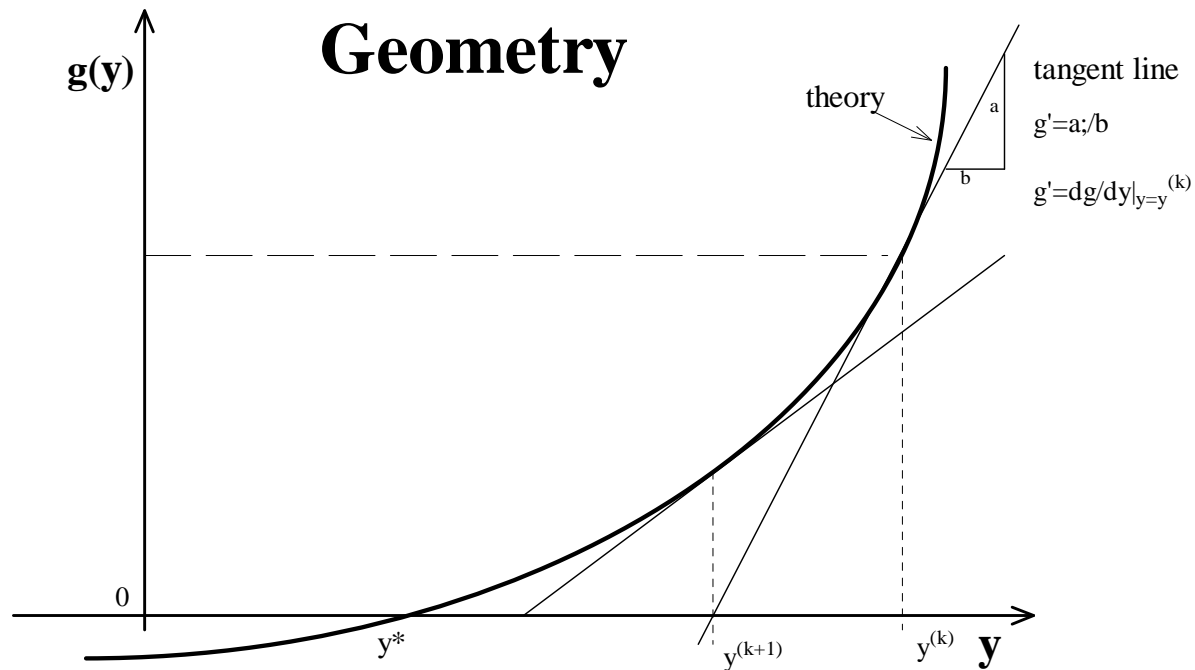The iterative process needs: $y^{(0)}$ —starting value.



Convergence

If g is twice differentiable and $\left. \frac{dg}{dy} \right|_{y=y^*} \neq \mathbf{0}$,

Then $\mathbf{y}^{(k)} \rightarrow \mathbf{y}^*$;

If $\mathbf{y}^{(0)}$ is sufficiently close to \mathbf{y}^* , the convergence is quadratic:

$$e_k = \left| \mathbf{y}^{(k)} - \mathbf{y}^* \right| \quad \text{and} \quad e_{k+1} \leq c e_k^2 \quad \text{where } c \text{—is a constant}$$

In constructing the iterative process we need a derivative. Numerical differentiation is “noisy” and thus we want to use analytical derivatives and avoid numerical differentiation.

4. Multivariable Newton-Raphson algorithm

Problem: find the solution to *the vector equation*: $f(\mathbf{x})=0$

where \mathbf{x} is *a vector* and $f(\mathbf{x})$ is *a vector function*.

Newton-Raphson iterations require *Jacobian*

$$\frac{\partial f}{\partial \mathbf{x}} = \mathbf{J}(\mathbf{x}) \quad .$$

The iterative process is constructed as follows

$$\mathbf{J}(\mathbf{x}^{(k)})\mathbf{x}^{(k+1)} = \mathbf{J}(\mathbf{x}^{(k)})\mathbf{x}^{(k)} - f(\mathbf{x}^{(k)})$$

where the Jacobian is computed via evaluation of partial derivatives.

The Jacobian is defined as follows:

$$J(\mathbf{x}^{(k)}) = \left. \frac{\partial f}{\partial \mathbf{x}} \right|_{\mathbf{x}=\mathbf{x}^{(k)}} = \begin{pmatrix} \frac{\partial f_1}{\partial x_1} & \cdots & \frac{\partial f_1}{\partial x_n} \\ \vdots & \ddots & \vdots \\ \frac{\partial f_n}{\partial x_1} & \cdots & \frac{\partial f_n}{\partial x_n} \end{pmatrix}_{\mathbf{x}=\mathbf{x}^{(k)}} \cdot$$

Multivariable N-R algorithm definitions:

the theoretical solution: $f(\mathbf{x}^*) = \mathbf{0}$ \mathbf{x}^* --solution

the iterative process:

$$J(\mathbf{x}^{(k)})\mathbf{x}^{(k+1)} = J(\mathbf{x}^{(k)})\mathbf{x}^{(k)} - f(\mathbf{x}^{(k)})$$

$$k = 0, 1, 2, \dots$$

Convergence conditions:

1. $J(\mathbf{x})$ is a LIPSCHITZ function: $\exists L$ such that if for $\forall \mathbf{x}, \mathbf{x}'$,
 $\|J(\mathbf{x}) - J(\mathbf{x}')\| \leq L\|\mathbf{x} - \mathbf{x}'\|$
2. $J(\mathbf{x}^*)$ is non-singular
3. If $\mathbf{x}^{[0]}$ is close enough to \mathbf{x}^* , then $\mathbf{x}^{(k)} \rightarrow \mathbf{x}^*$ when $k \rightarrow \infty$.

Observations:


a.) Good estimates of initial (starting) values are important.

In case of difficulties we use: Source stepping

The algorithm is based on the assumption that circuit variables are 0 if sources are 0.

b. Device models must be continuous with continuous partial derivatives.

5. Examples_Exercises

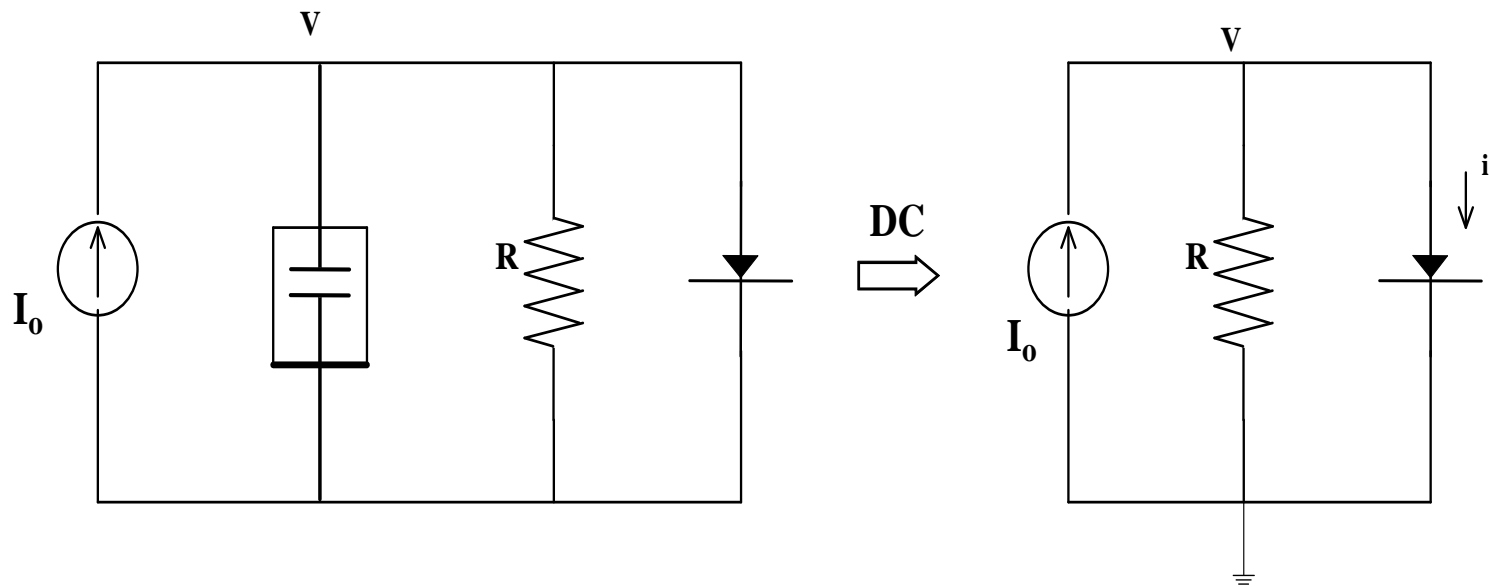

$$\text{CE: } i = I_s \left(e^{\frac{v}{V_t}} - 1 \right) = \bar{g}(v)$$

$$\text{KCL: } I_o = \frac{1}{R} V + i$$

Equation to be solved (D-C) is non-linear:

$$I_o - \frac{V}{R} = I_s (e^{\frac{V}{V_t}} - 1)$$

We construct an iterative procedure with $V^{(k)}$ – as a starting value.

Exercise 1:

a.) Derive iterative equation

$$I_o - \frac{1}{R} V^{(k+1)} = I_s (e^{\frac{V^{(k)}}{V_t}} - 1) + \frac{I_s}{V_t} e^{\frac{V^{(k)}}{V_t}} (V^{(k+1)} - V^{(k)})$$

$$k = 0, 1, 2, \dots$$

b.) Assume: $I_o = 1[mA]$, $R = 40[k\Omega]$, $I_s = 2.5 \cdot 10^{-12}[A]$;

Calculate the first three steps (k=1,2,3) of the iteration process starting at two different starting points:

- 1) $V^{[0]}=0$
- 2) $V^{[0]}=0.5 [V]$

Example of non-convergence in analysis of an operational amplifier

$$k = 1$$

$$\|V^{(1)} - V^{(0)}\| = 5$$

after $k=100$ (default in SPICE), **no convergence** message was issued.

Try the following brute force approach (increase the iteration limit – ITL1):

.OPTION , **ITL1=1000**,

Results

.....

.....

$$k = 666$$

$$\|V^{(666)} - V^{(665)}\| = 43.02 \cdot 10^3 [V]$$

.....

.....

$$k = 675$$

$$\|V^{(675)} - V^{(674)}\| = 0.25 \cdot 10^{-2} [V]$$

Convergence!

6. Modifications to Newton-Raphson algorithm

Limiting equations

Example of diode: $i = I_s (e^{\frac{V}{V_t}} - 1)$

$$V = V_{Lim} \Rightarrow i = i_{mx}$$

$$i_{mx} = I_s e^{\frac{V_{Lim}}{V_t}} \quad V_{Lim} \gg V_{tx}$$

$$V_{Lim} = V_t \ln\left(\frac{i_{mx}}{I_s}\right)$$

In the iterations:

If $V^{(k+1)} > V_{Lim}$

then

$$\bar{V}^{(k+1)} = V_{Lim} \cdot$$

Modification to an iterative process will be discussed.

Notation:

V_0 --starting point

\hat{V}_1 --computed new point

V_1 --accepted new point.

Three examples of specific procedures:

A.)Fixed departures in voltage

Procedure:

1. $V_0 < 10V_t$ and $\hat{V}_1 < 10V_t$ then $V_1 = \hat{V}_1$

2. $\left| V_0 - \hat{V}_1 \right| \leq 2V_t$ then $V_1 = \hat{V}_1$

3. $V_0 > 10V_t$ and $\hat{V}_1 < V_0$ then $V_1 = V_0 - 2V_t$

4. $\hat{V}_1 > V_0$ and $\hat{V}_1 > 10V_t$ then $V_1 = \max\{10V_t, V_0 + 2V_t\}$

B) Non-linearly limited departures


$$V_1 = V_0 + 10V_t \cdot \overline{\overline{\tanh}}\left(\frac{\hat{V}_1 - V_0}{10V_t}\right)$$

the $\overline{\overline{\tanh}}(\)$ is approximated as follows:


$$\overline{\overline{\tanh}}(x) = \begin{cases} \pm 1 & |x| > \frac{3}{2} \\ x - \frac{x^3}{3} & \frac{1}{2} < |x| \leq \frac{3}{2} \\ x & |x| \leq \frac{1}{2} \end{cases}$$

Note that when $|x| \leq \frac{1}{2}$ than $V_1 = \hat{V}_1$.


Graphical illustration

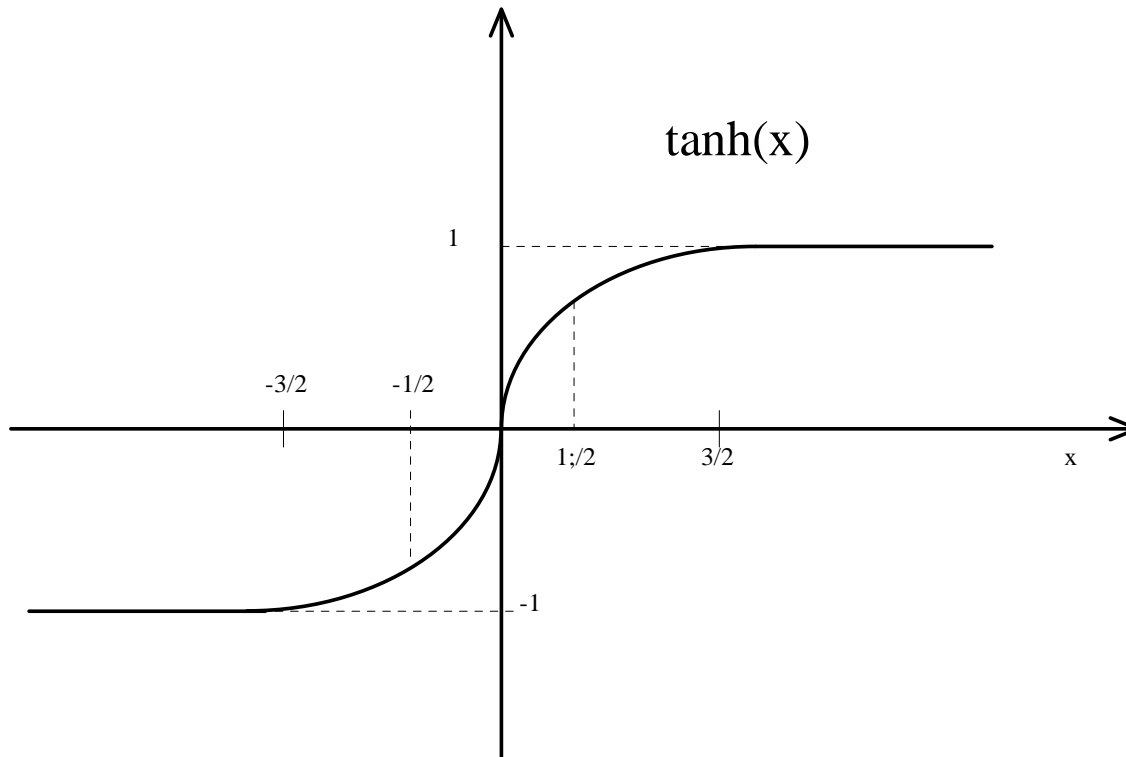

C) Iterating in voltage or current

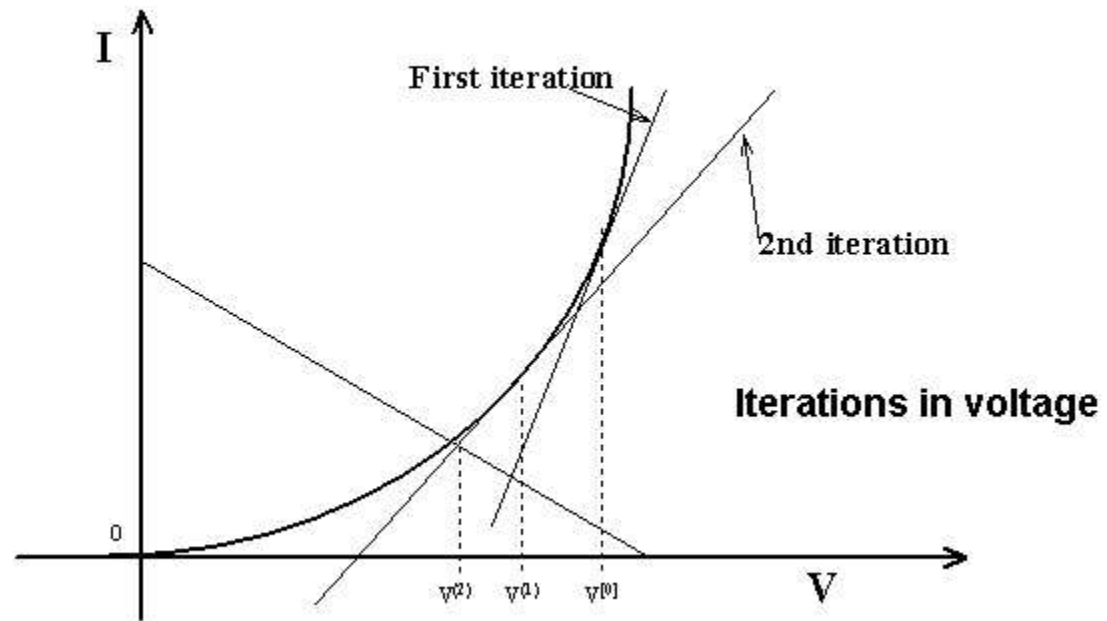


Iteration in current

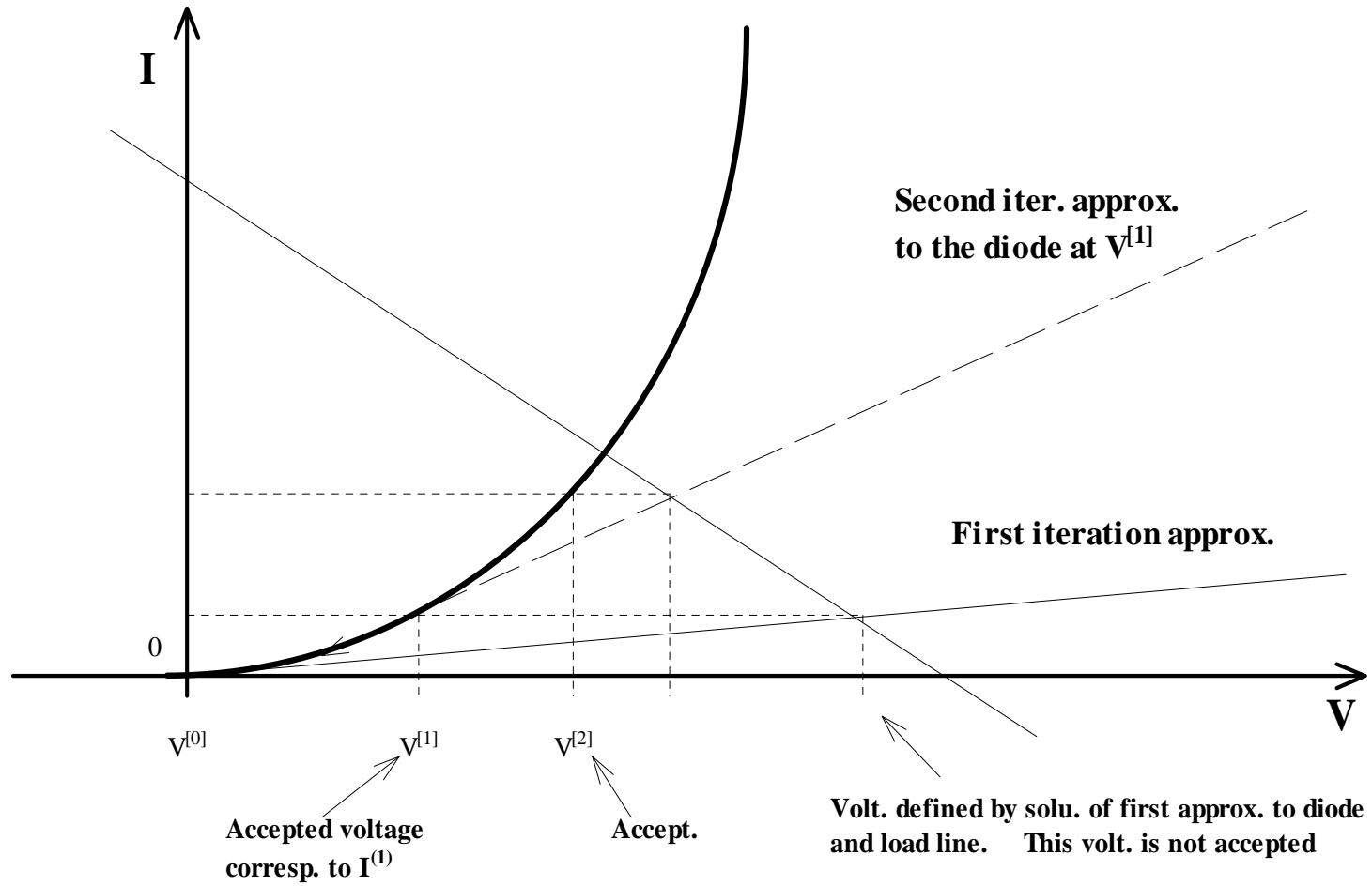

Linearized relations
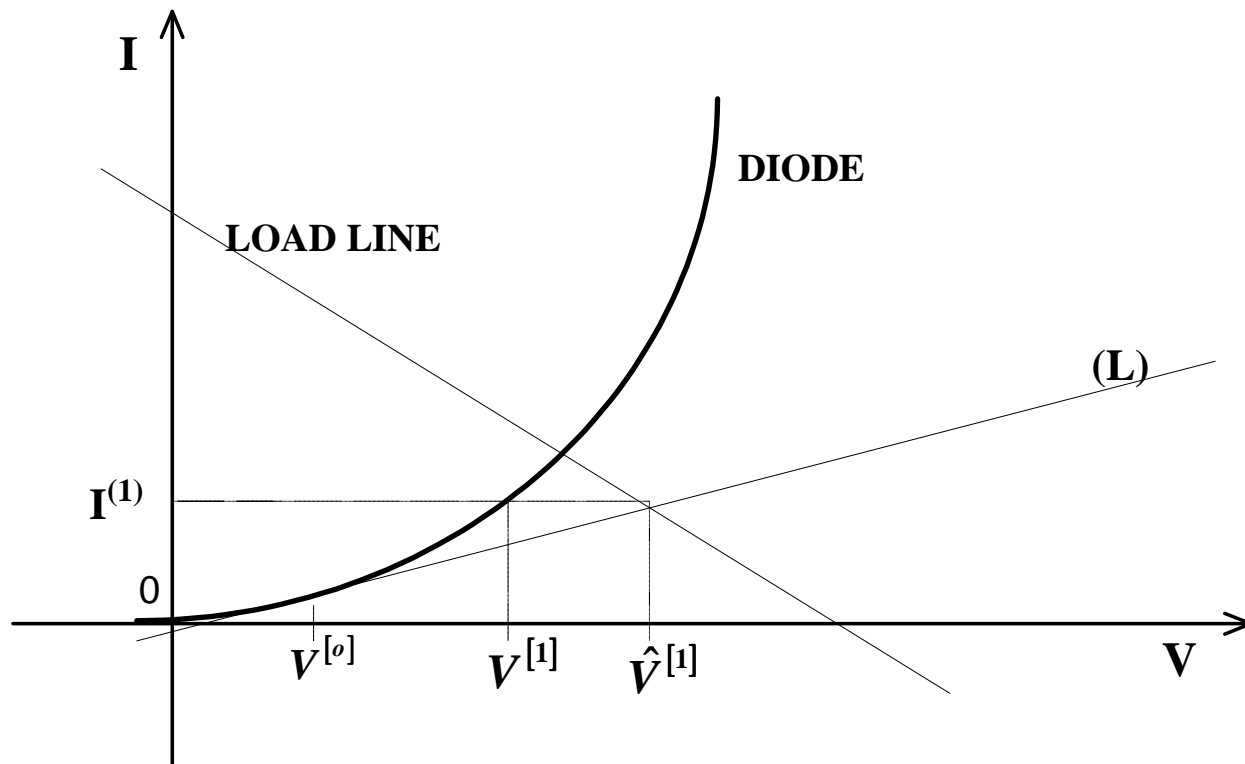
$$\hat{I} = I_s \left(e^{\frac{V^{(o)}}{V_t}} - 1 \right) + \frac{I_s}{V_t} e^{\frac{V^{(o)}}{V_t}} (\hat{V}^{(1)} - V^{(o)}) \quad (\text{L})$$



$$\hat{I} = I^{(1)} \quad \text{in (L)}$$

$$\text{(Diode)} \quad I^{(1)} = I_s \left(e^{V^{(1)}/V_t} - 1 \right) \Rightarrow v^{(1)}$$

Note: $I^{(1)}$ is defined by the intersection of (L) and load lines

After algebra (do as an exercise)

$$V^{(1)} = V^{(0)} + V_t \ln\left(1 + \frac{\hat{V}^{(1)} - V^{(0)}}{V_t}\right)$$

When to iterate in current or when to iterate in voltage?

Find V_{crit}

$$\hat{V}^{(k+1)} < V_{crit} \quad \text{iterate in current}$$

$$\hat{V}^{(k+1)} > V_{crit} \quad \text{iterate in voltage}$$

Critical current (arbitrary choice of value is given below).

Critical current is determined as a current caused by the thermal voltage, V_t , applied to the resistor of $\sqrt{2}[\Omega]$.

$$I_{crit} = \frac{V_t}{\sqrt{2}} \quad \text{this is an arbitrary definition}$$

$$I = I_s (e^{V/V_t} - 1) \quad \frac{V_{crit}}{V_t} \gg 1$$

$$I_{crit} = I_s e^{V_{crit}/V_t}$$

⇓

$$V_{crit} = V_t \ln\left(\frac{V_t}{\sqrt{2}I_s}\right)$$

Exercise:

Calculate the first 3 steps in iteration for D-C analysis (use circuit specified in the exercise 1) using the following algorithms:

1. fixed departures in voltage.
2. nonlinearly limited departures
3. iteration in current or voltage as necessary (as indicated by V_{crit}).

Assume $V^{(0)}=0$ as a starting point.

7. DC convergence control in SPICE

Control parameters:

RELTOL	default value is 10^{-3}
ABSTOL	default value is 1 [pA]
VNTOL	default value is 1 [μV]

Convergence criterion

$$\|x^{(k+1)} - x^{(k)}\| \leq \varepsilon_a + \varepsilon_r \max\{\|x^{(k)}\|, \|x^{(k+1)}\|\}$$

where ε_a represents ABSTOL or VNTOL

ε_r represents RELTOL.

Other parameters:

ITL1-sets the limit for the number of iterations in DC analysis,

the default number is 100,

ITL2-sets the limit for the number of iterations in computing the transfer curve

the default number is 50.

Details of convergence control in SPICE

A. circuit variables –convergence criteria

--nodal voltages

$$\left| \mathbf{v}_n^{(k+1)} - \mathbf{v}_n^{(k)} \right| \leq \mathbf{VNTOL} + \mathbf{RELTOL} \cdot \max\left\{ \left| \mathbf{v}_n^{(k+1)} \right|, \left| \mathbf{v}_n^{(k)} \right| \right\}$$

--branch currents (computation of I_2 vector)

$$\left| \mathbf{i}_\ell^{(k+1)} - \mathbf{i}_\ell^{(k)} \right| \leq \mathbf{ABSTOL} + \mathbf{RELTOL} \cdot \max\left\{ \left| \mathbf{i}_\ell^{(k+1)} \right|, \left| \mathbf{i}_\ell^{(k)} \right| \right\}$$

B. I-V characteristics (functions like: I_D (diode); I_B (BJT); I_{DS} (FET))

Example of criterion for diode:

Notation: V_J —junction voltage

Current due to the voltage value determined in the previous (k^{th} —iteration)

$$I_D = I_S \left(e^{\frac{V_J^{(k)}}{V_t}} - 1 \right)$$

Current from the linearized equation ($k+1$ ---iter.)

$$\tilde{I}_D = \frac{I_S}{V_t} e^{\frac{V_J^{(k)}}{V_t}} V_J^{(k+1)} + I_D - \frac{I_S}{V_t} e^{\frac{V_J^{(k)}}{V_t}} V_J^{(k)}$$

convergence criterion for I-V relations

$$|\tilde{I}_D - I_D| \leq \text{ABSTOL} + \text{RELTOL} \cdot \max\{I_D, \tilde{I}_D\}$$

Convergence criteria for circuit variables and I-V relations must be satisfied in:

ITL1 —iterations for D-C analysis

ITL2—iterations for D-C transfer curve.

8. Concluding remarks

D-C analysis is performed before the following major analyses:

AC, TRAN, SENS, TRANSF. CURVES

unless it is cancelled by a user.

Sensitivity analysis

.SENS outvar *computes sensitivity of “outvar” with respect to every element in the circuit and all D-C parameters of diodes and BJT’s (FET’s are excluded)*

Generation of D-C transfer curves (example: I-V)

DC Vname start stop step <vname1 strt1 stp1 setp1....>

Help/suggestions for dealing with convergence problems.

1. Nothing helps better than knowledge of circuit and setting good starting values using **NODESET** **V(node)=value < V(node1)=value1.....>**
2. Check tolerances (defaults) and possibly relax them.
3. Increase **ITL1**—limit for the number of iterations in **DC** analysis.
4. Use source ramping (this is automatically initiated in SPICE3 & PSPICE), in SPICE2 one must set **ITL6=.....(50)**.
5. Use “off” flag at the end of transistor lines to indicate the transistors that may be turned off.

To learn more about the computing process, use **ACCT** option, which gives some additional numerical details.

When **DC** analysis converges, one can use the flag

.OP - which is a request for operating point information such as:

1. the terminal currents & voltages;
2. the small signal equivalent conductances for all Non-Linear devices.

The information is listed in the “**OPERATING POINT INFO**” section of the output.

Note: **.OP** is done by default when **.DC** is not followed by any analysis specification.